

The background features abstract, colorful swirls in shades of green, blue, and purple, interspersed with small yellow triangles.

Alexander-Sadiku

Fundamentals of Electric Circuits

Chapter 2

Basic Laws

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Basic Laws - Chapter 2


- 2.1 Ohm's Law.
- 2.2 Nodes, Branches, and Loops.
- 2.3 Kirchhoff's Laws.
- 2.4 Series Resistors and Voltage Division.
- 2.5 Parallel Resistors and Current Division.
- 2.6 Wye-Delta Transformations.

2.1 Ohms Law (1)

- Ohm's law states that the voltage across a resistor is directly proportional to the current I flowing through the resistor.
- Mathematical expression for Ohm's Law is as follows:

$$v = iR$$

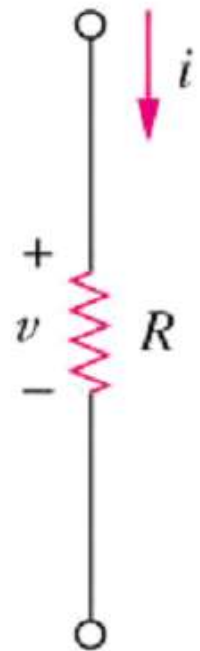- Two extreme possible values of R : **0 (zero)** and ∞ (**infinite**) are related with two basic circuit concepts: **short circuit** and **open circuit**.



2.1 Ohms Law (2)

- Conductance is the ability of an element to conduct electric current; it is the reciprocal of resistance R and is measured in mhos or siemens.

$$G = \frac{1}{R} = \frac{i}{v}$$

- The power dissipated by a resistor:

$$p = vi = i^2 R = \frac{v^2}{R}$$



2.2 Nodes, Branches and Loops (1)

- A **branch** represents a single element such as a voltage source or a resistor.
- A **node** is the point of connection between two or more branches.
- A **loop** is any closed path in a circuit.
- A network with b branches, n nodes, and l independent loops will satisfy the fundamental theorem of network topology:

$$b = l + n - 1$$

2.2 Nodes, Branches and Loops (2)

Example 1

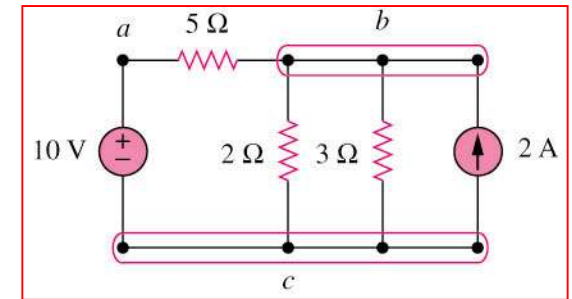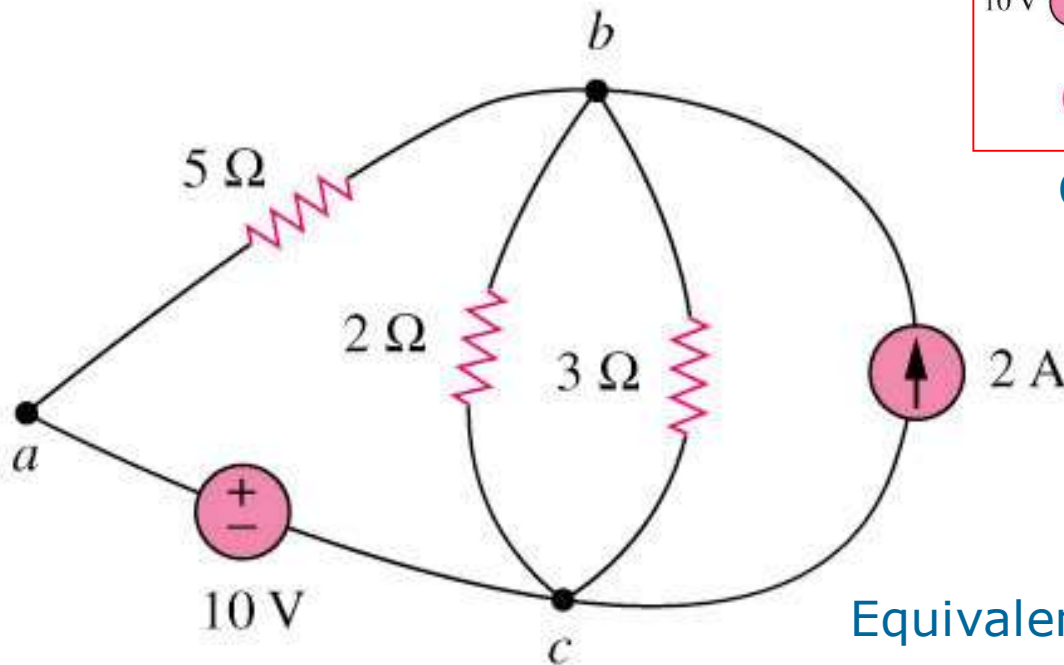

Original circuit


Equivalent circuit

How many branches, nodes and loops are there?

2.2 Nodes, Branches and Loops (3)

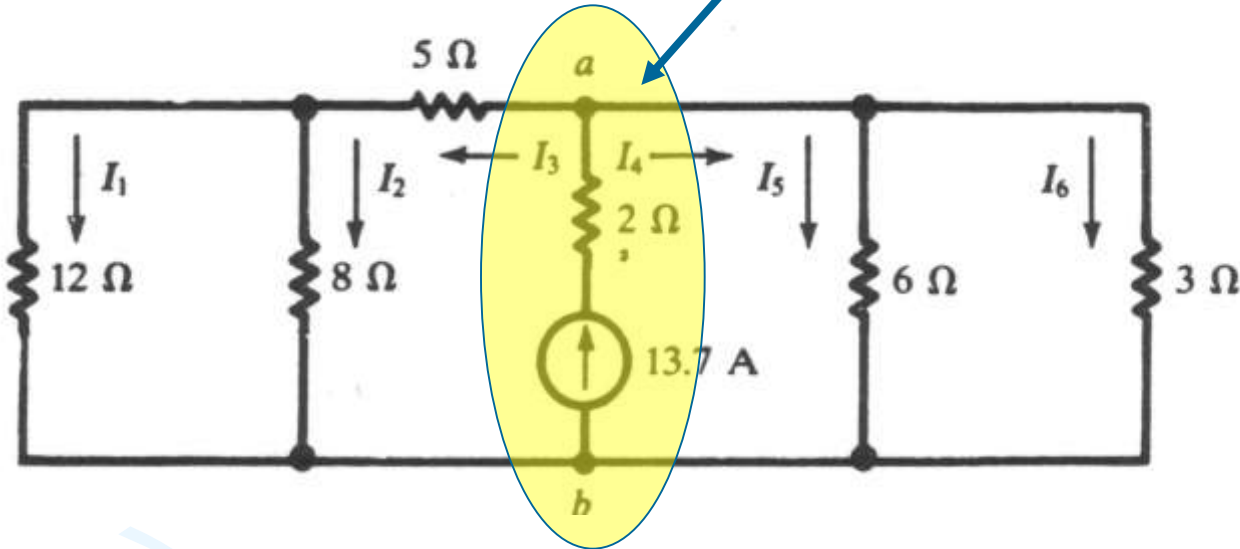Example 2


Should we consider it as one branch or two branches?



How many branches, nodes and loops are there?

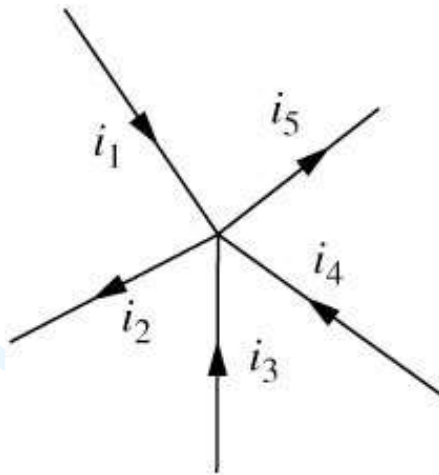
2.3 Kirchhoff's Laws (1)

- Kirchhoff's current law (KCL) states that the algebraic sum of currents entering a node (or a closed boundary) is zero.



Mathematically,


$$\sum_{n=1}^N i_n = 0$$

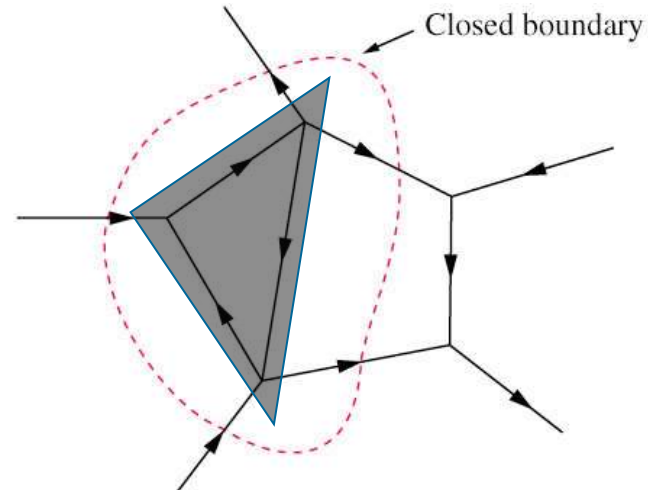

2.3 Kirchhoff's Laws (2)

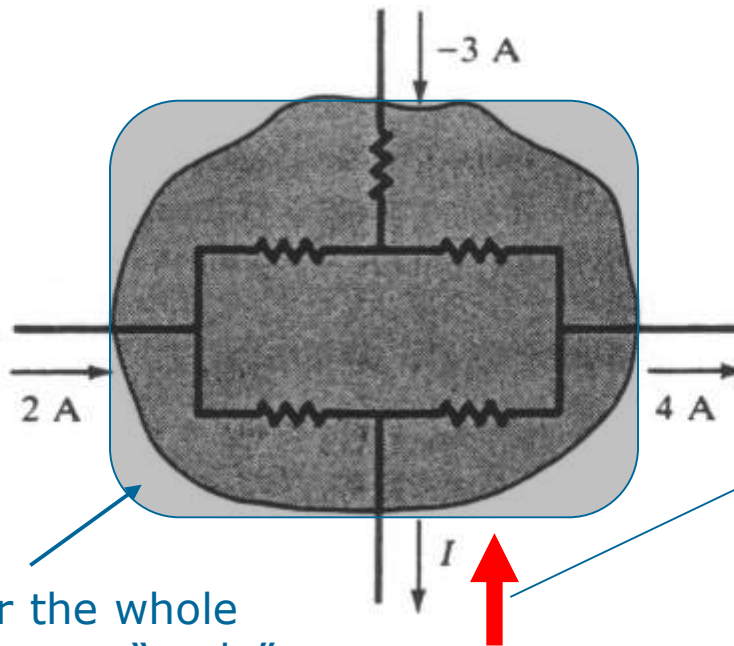Example 4

- Determine the current I for the circuit shown in the figure below.



$$I + 4 - (-3) - 2 = 0$$


$$\Rightarrow I = -5\text{ A}$$

This indicates that the actual current for I is flowing in the opposite direction.

We can consider the whole enclosed area as one "node".

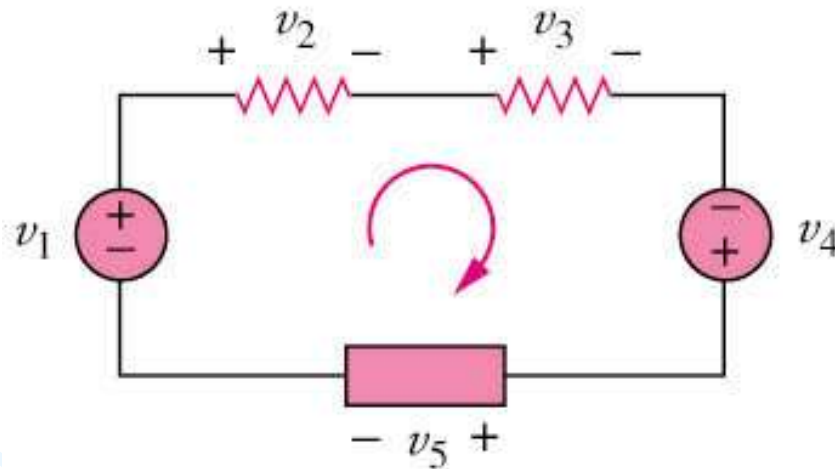2.3 Kirchhoff's Laws (3)

- Kirchhoff's voltage law (KVL) states that the algebraic sum of all voltages around a closed path (or loop) is zero.




Mathematically,

$$\sum_{m=1}^M v_n = 0$$

2.3 Kirchhoff's Laws (4)

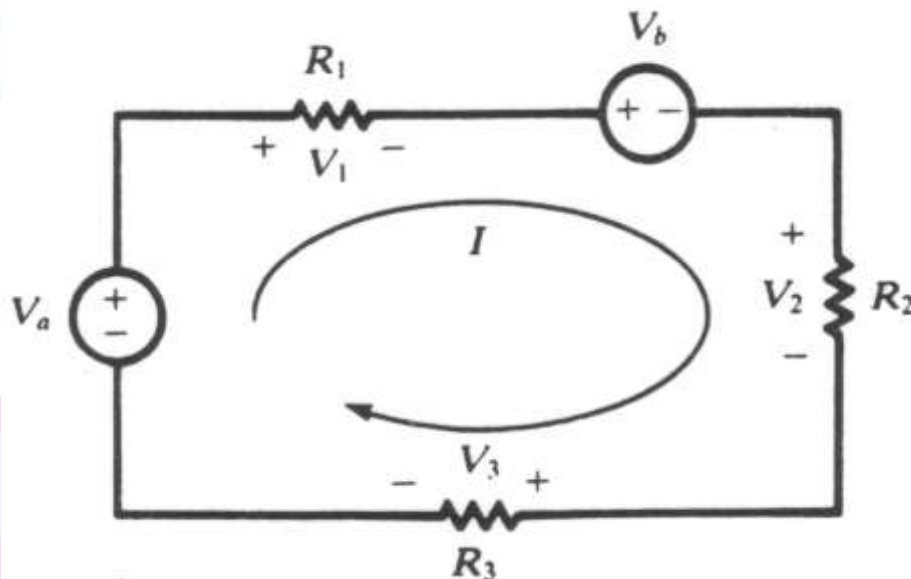Example 5

- Applying the KVL equation for the circuit of the figure below.



$$V_a - V_1 - V_b - V_2 - V_3 = 0$$

$$V_1 = IR_1 \quad V_2 = IR_2 \quad V_3 = IR_3$$

$$\Rightarrow V_a - V_b = I(R_1 + R_2 + R_3)$$

$$I = \frac{V_a - V_b}{R_1 + R_2 + R_3}$$

2.4 Series Resistors and Voltage Division (1)

- Series: Two or more elements are in series if they are cascaded or connected sequentially and consequently carry the same current.
- The equivalent resistance of any number of resistors connected in a series is the sum of the individual resistances.


$$R_{eq} = R_1 + R_2 + \cdots + R_N = \sum_{n=1}^N R_n$$

- The voltage divider can be expressed as

$$v_n = \frac{R_n}{R_1 + R_2 + \cdots + R_N} v$$

2.4 Series Resistors and Voltage Division (1)

Example 3

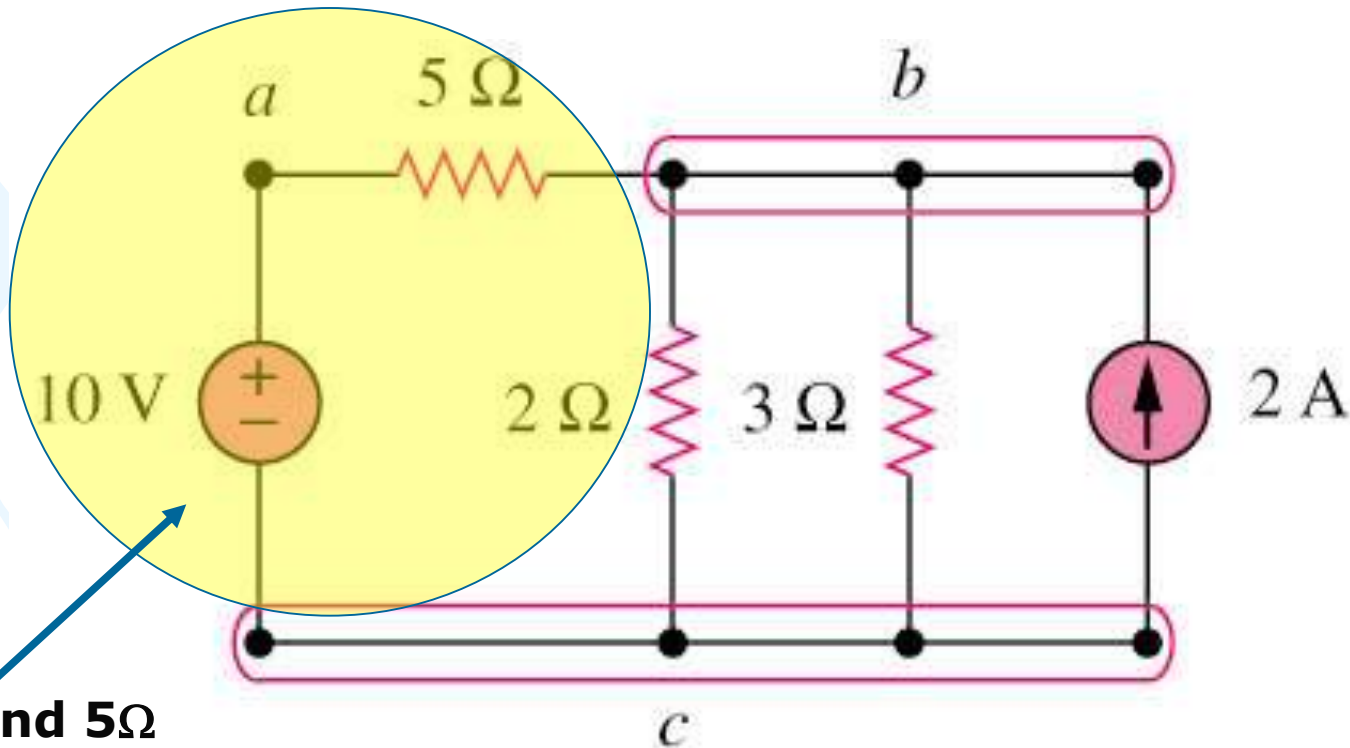

**10V and $5\ \Omega$
are in series**

2.5 Parallel Resistors and Current Division (1)

- Parallel: Two or more elements are in parallel if they are connected to the same two nodes and consequently have the same voltage across them.
- The equivalent resistance of a circuit with N resistors in parallel is:


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$

- The total current i is shared by the resistors in inverse proportion to their resistances. The current divider can be expressed as:

$$i_n = \frac{v}{R_n} = \frac{iR_{eq}}{R_n}$$

2.5 Parallel Resistors and Current Division (1)

Example 4

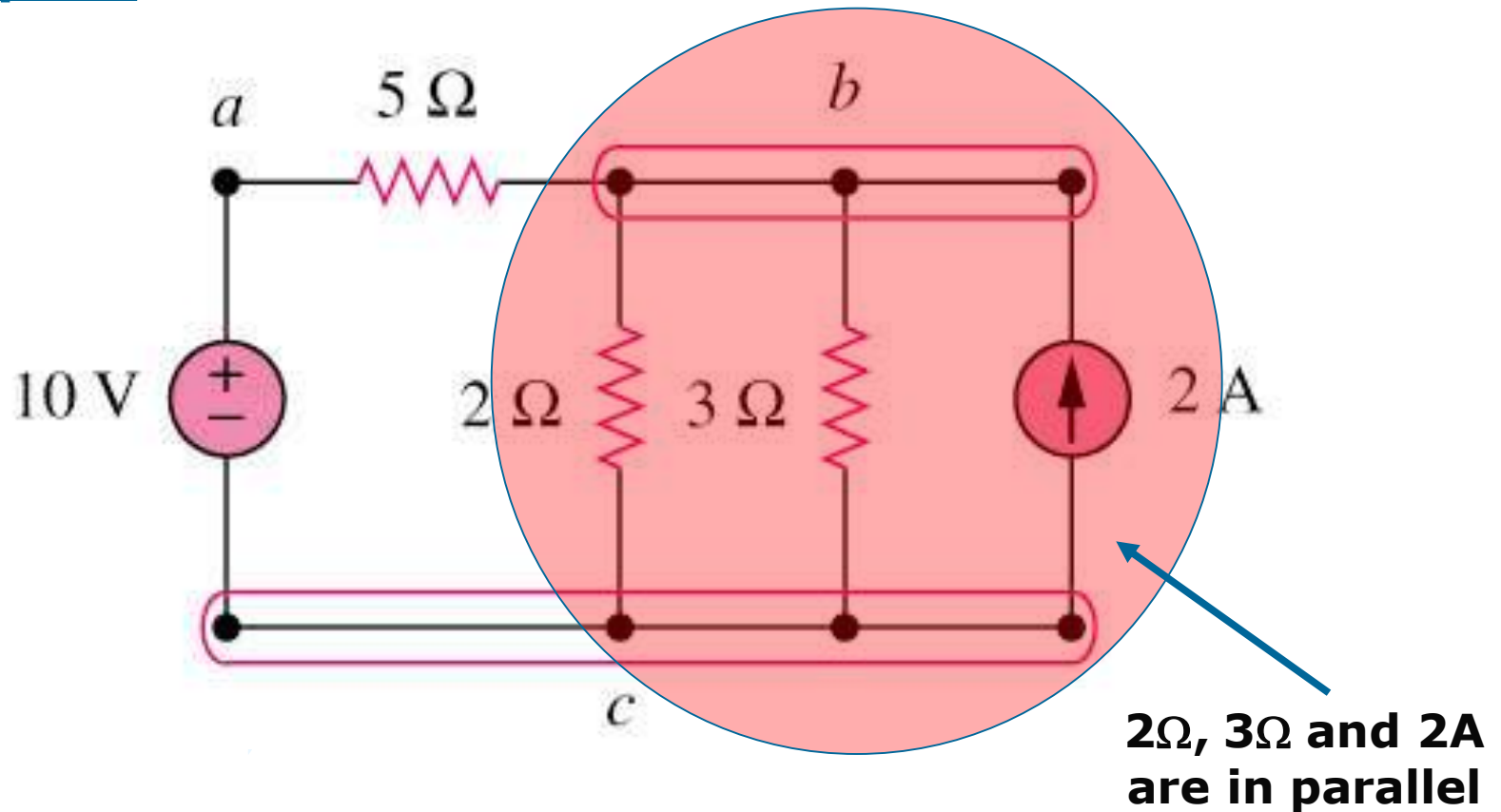


2.6 Wye-Delta Transformations

Delta -> Star

$$R_1 = \frac{R_b R_c}{(R_a + R_b + R_c)}$$

$$R_2 = \frac{R_c R_a}{(R_a + R_b + R_c)}$$
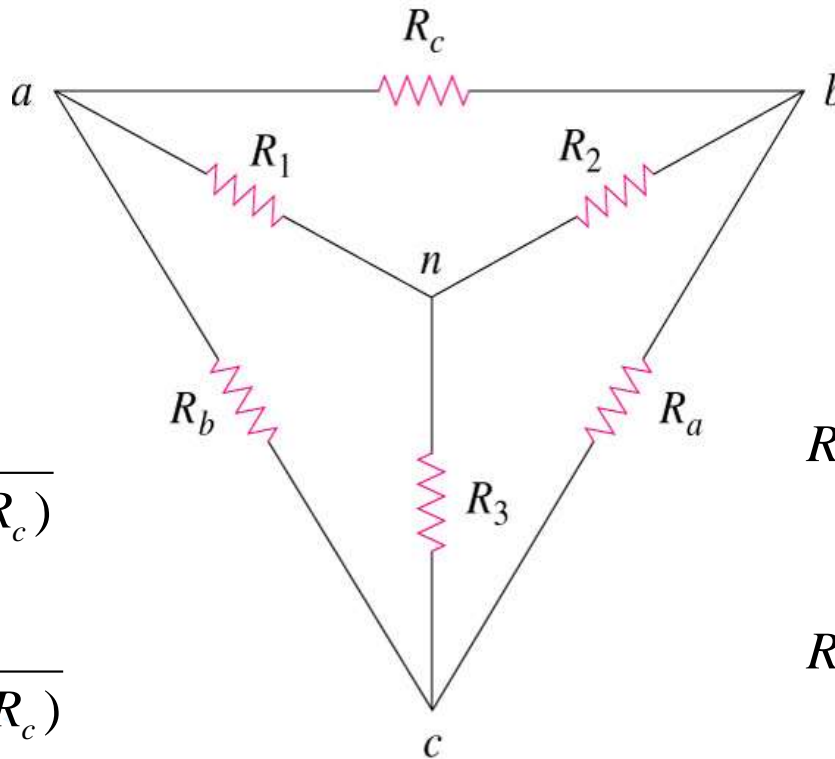
$$R_3 = \frac{R_a R_b}{(R_a + R_b + R_c)}$$



Star -> Delta

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$