

**EAST  
WEST  
UNIVERSITY**



**Electrical Circuit (CSE209)**

Lab Report

Experiment – 3

Submitted to

**M. Saddam Hossain Khan**

Senior Lecturer

Department of Computer Science & Engineering

Submitted by

Name: **Ishfaf Zaman Khan**

Student ID: **2023-3-60-338**

Section: 02

Date: 25<sup>th</sup> March, 2025

**Pre-Lab Marks:**

**Post-Lab Marks:**


**Total Marks:**

**Experiment Name: Bias Point Details Analysis of DC Circuit with Independent Sources Using PSpice Schematics.**

**Objectives:**

1. To learn the fundamentals of PSpice
2. To analyze the Bias Point Detail of the DC circuit using PSpice schematics.

**Circuit Diagram:**

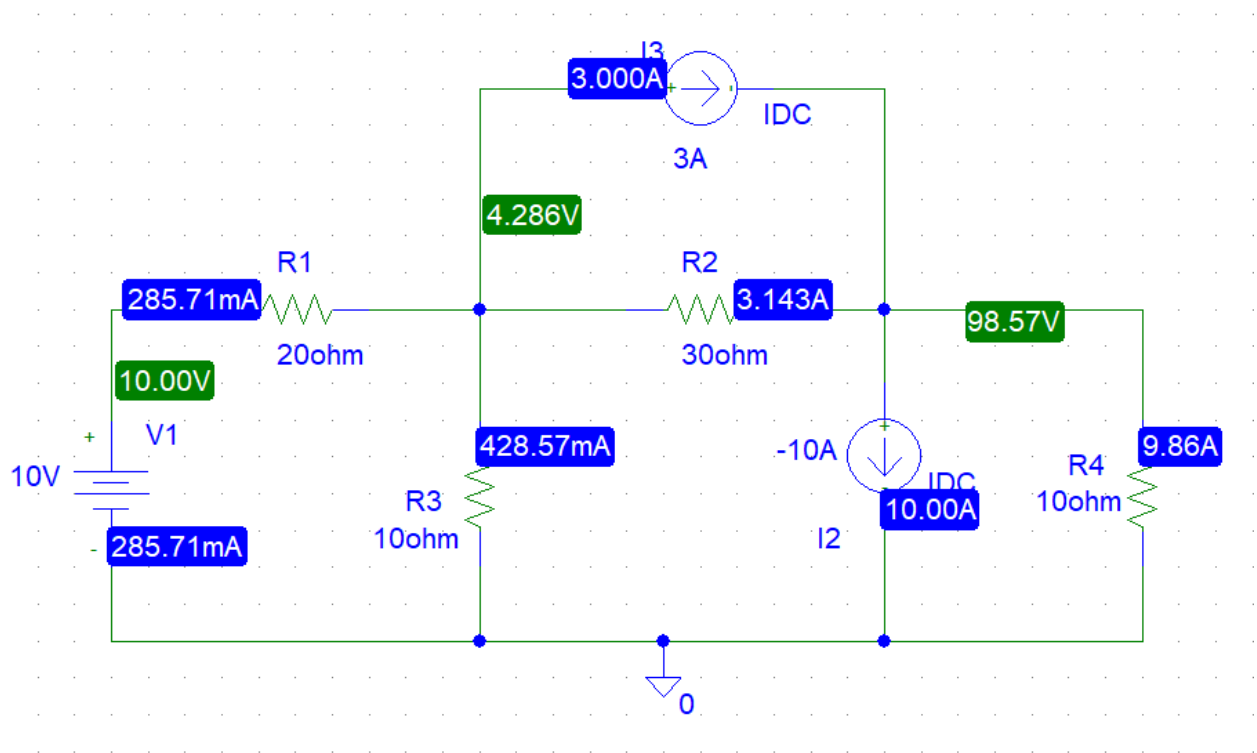

**Figure-2**

**Schematics Netlist:**

```
I_I3      $N_0001 $N_0002 DC 3A
R_R4      0 $N_0002 10ohm
R_R3      0 $N_0001 10ohm
R_R2      $N_0001 $N_0002 30ohm
```

R\_R1      \$N\_0003 \$N\_0001 20ohm  
V\_V1      \$N\_0003 0 10V  
I\_I2      \$N\_0002 0 DC -10A

### Post-Lab Questions

**1. Theoretically calculate all the currents and the voltages for the circuit shown in Figure 2.**

Solution:

From figure 02,

$$i_2 = -10A$$

$$i_3 = 3A$$

Now,

As VDC is in between node 1 and 0 so,

$$V_1 = 10V$$

Applying KCL and Ohm's law at nodes 2 and 3,

$$\frac{10 - V_2}{20} = \frac{V_2}{10} + \frac{V_2 - V_3}{30} + 3$$

$$\text{Or, } \frac{10 - V_2}{2} - V_2 - \frac{V_2 - V_3}{3} = 30$$

$$\text{Or, } \frac{30 - 3V_2 - 6V_2 - 2V_2 + 2V_3}{6} = 30$$

$$\therefore -11V_2 + 2V_3 = 150 \dots\dots\dots(i)$$

And,

$$\frac{V_2 - V_3}{30} + 3 = -10 + \frac{V_3}{10}$$

$$\text{Or, } \frac{V_2 - V_3}{3} - V_3 = -100 - 30$$

$$\text{Or, } \frac{V_2 - V_3 - 3V_3}{3} = -130$$

$$\therefore V_2 - 4V_3 = -390 \dots\dots\dots(ii)$$

From (ii),

$$V_2 = -390 + 4V_3 \dots\dots\dots(iii)$$

Substituting  $V_2 = -390 + 4V_3$  in equation (i),

$$-11(-390 + 4V_3) + 2V_3 = 150$$

$$\text{Or, } 4290 - 44V_3 = 150$$

$$\text{Or, } -42V_3 = -4140$$

$$\therefore V_3 = 98.57$$

Substituting  $V_3 = 98.57V$  in equation (iii),

$$V_2 = -390 + 4 \times 98.57 = 4.286V$$

By solving equations (i) and (ii) we get,

$$V_2 = 4.286V$$

$$V_3 = 98.57V$$

Now,

$$i_2 = \frac{10 - V_2}{20} = \frac{10 - 4.286}{20} A = 0.2857A = 258.7mA$$

$$i_4 = \frac{V_3}{10} = \frac{98.57}{10} A = 9.857A$$

$$i_5 = \frac{V_2 - V_3}{30} = \frac{4.286 - 98.57}{30} = -3.143A$$

$$i_6 = \frac{V_2}{10} = \frac{4.286}{10} A = 0.4286A = 428.6mA$$

So the values are,

$$i_1 = 258.7\text{mA}$$

$$i_2 = -10\text{A}$$

$$i_3 = 3\text{A}$$

$$i_4 = 9.858\text{A}$$

$$i_5 = -3.143\text{A}$$

$$i_6 = 428.6\text{mA}$$

And,

$$V_1 = 10\text{V}$$

$$V_2 = 4.286\text{V}$$

$$V_3 = 98.57\text{V}$$

**2. Compare the theoretical solution of the circuit shown in the figure with the solutions obtained from PSpice.**

Solution:

Comparing values of voltages,

PSpice	Theoretical
<b><math>V_1 = 10\text{ V}</math></b>	<b><math>V_1 = 10\text{ V}</math></b>
<b><math>V_2 = 4.286\text{ V}</math></b>	<b><math>V_2 = 4.286\text{ V}</math></b>
<b><math>V_3 = 98.57\text{ V}</math></b>	<b><math>V_3 = 98.57\text{ V}</math></b>

Comparing the values of current,

PSpice	Theoretical
$i_1 = 258.71\text{ mA}$	$i_1 = 258.71\text{ mA}$

$i_2 = -10 \text{ A}$	$i_2 = -10 \text{ A}$
$i_3 = 3 \text{ A}$	$i_3 = 3 \text{ A}$
$i_4 = 9.86 \text{ A}$	$i_4 = 9.86 \text{ A}$
$i_5 = -3.143 \text{ A}$	$i_5 = -3.143 \text{ A}$
$i_6 = 428.57 \text{ mA}$	$i_6 = 428.57 \text{ mA}$

All the values of currents and voltages we get theoretically, and from PSpice, are equal.

### Discussion:

1. The components in the schematic must be placed in the correct order, following the circuit diagram.
2. The values of resistances, voltages, and currents should be changed according to the given values in the manual.
3. The circuit should use proper grounding to avoid simulation errors or incorrect results.
4. The applications of PSpice simulation should be learned from this experiment.
5. It is needed to calculate accurately to get the exact theoretical values.

### Conclusion:

This experiment successfully analyzed the DC circuit's bias point using theoretical calculations and PSpice simulations. The close match between calculated and simulated values confirmed the accuracy of both methods. It also demonstrated the importance of circuit analysis techniques and the usefulness of simulation tools in verifying theoretical results.