




EAST WEST UNIVERSITY
 Department of Computer Science and Engineering
 B.Sc. in Computer Science and Engineering Program
 Mid Term 2, Summer 2021


Course: CSE 109/209 – Electrical Circuits, Section-4
 Instructor: SHK, Senior Lecturer, CSE Department
 Full Marks: 40
 Time: 1 Hour and 30 Minutes [Including attachment time]

Note: There are FIVE questions, answer ALL of them. Course outcomes (CO), and marks of each question are mentioned at the right margin.

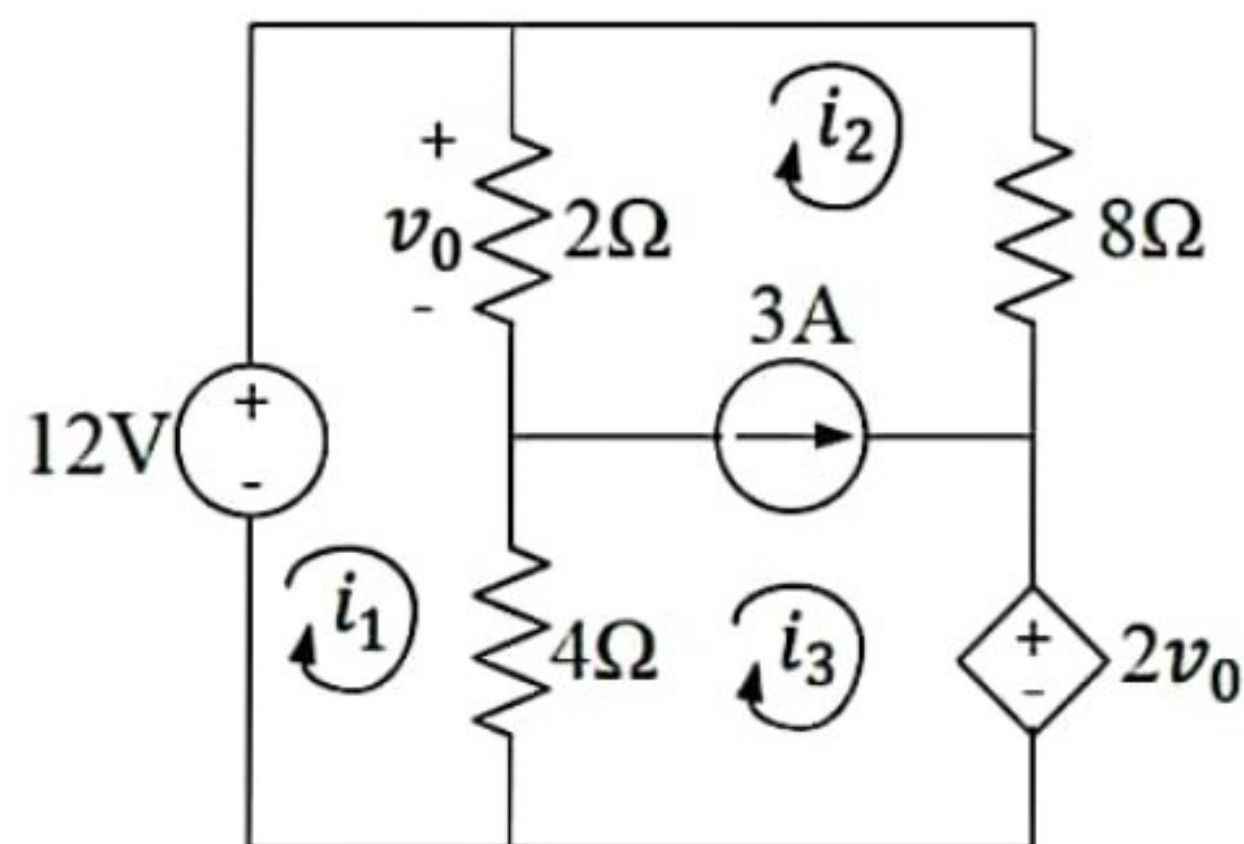
1. Using mesh currents indicated in the circuit, determine i_1 , i_2 and i_3 in the following circuit. [CO2, Mark:12]



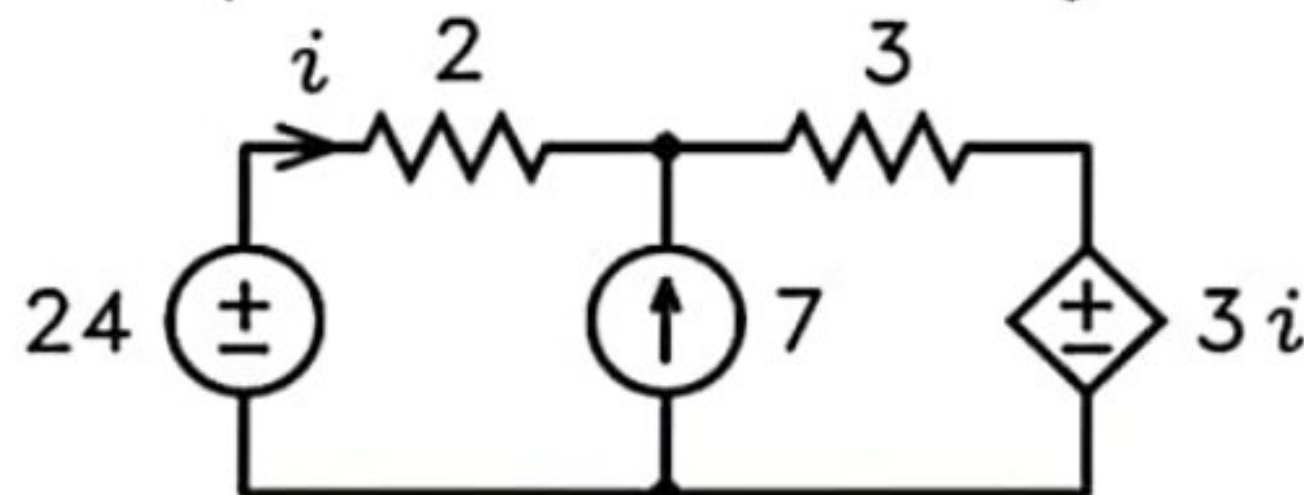
2. Use superposition technique to determine i in the following circuit. [CO2, Mark: 8]



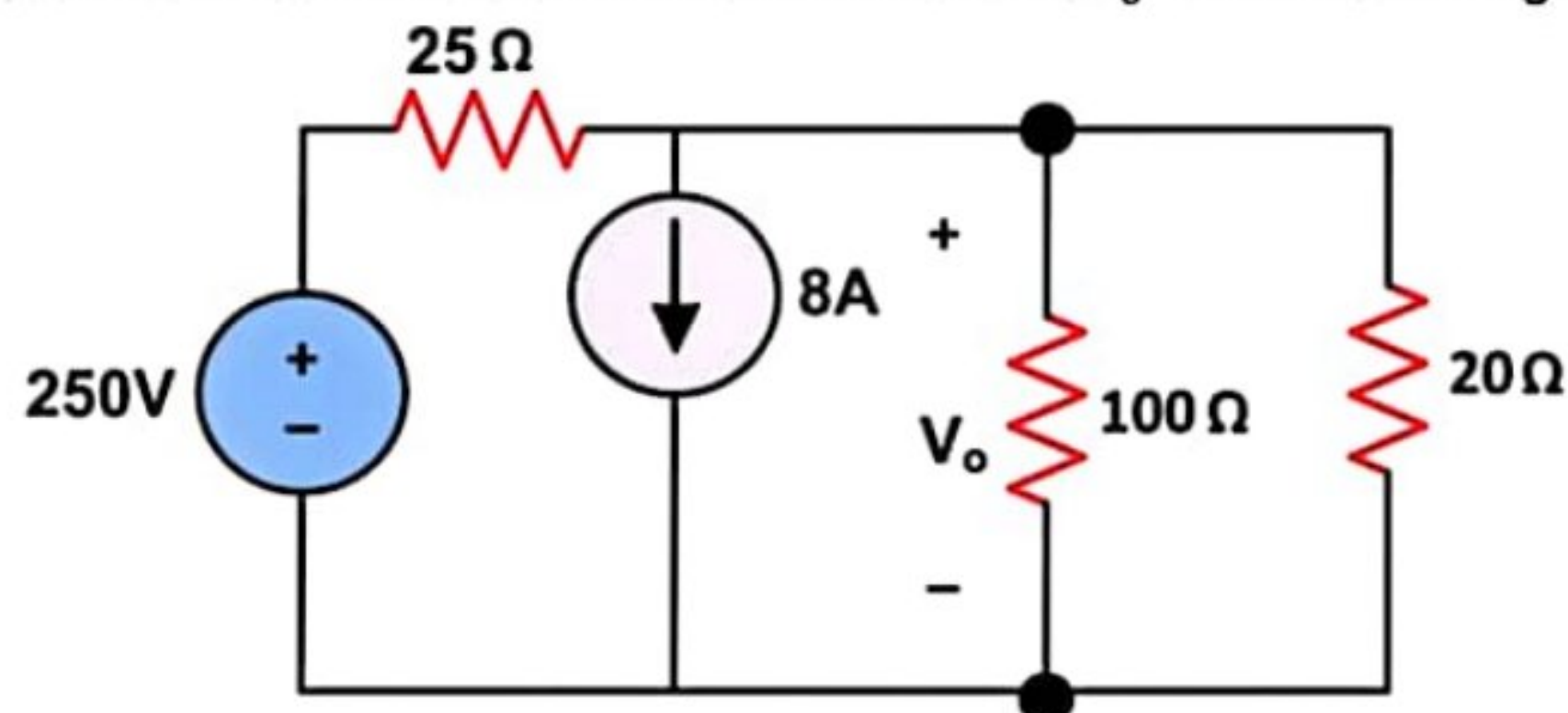
3. Use most effective source transformation to determine V_o in the following circuit. [CO2, Mark: 6]



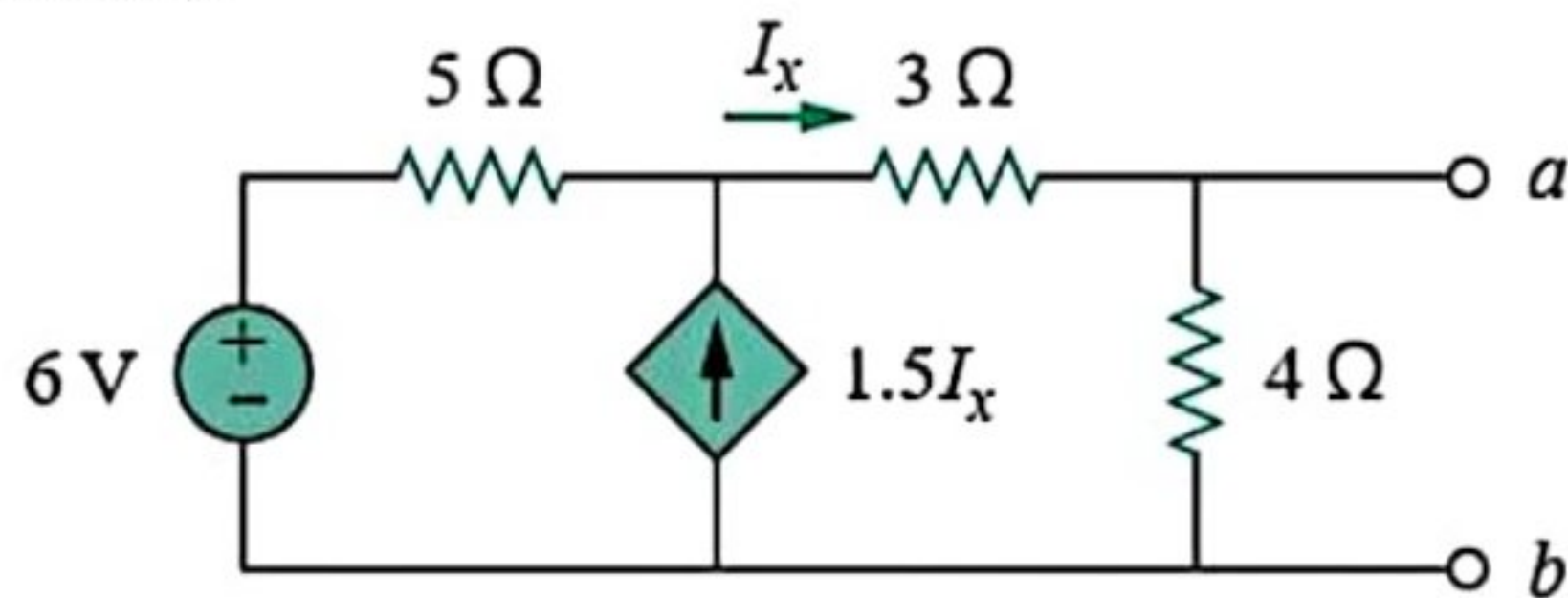4. Determine the Thevenin equivalent of the following circuit with respect to terminals a and b . [CO2, Mark:6]



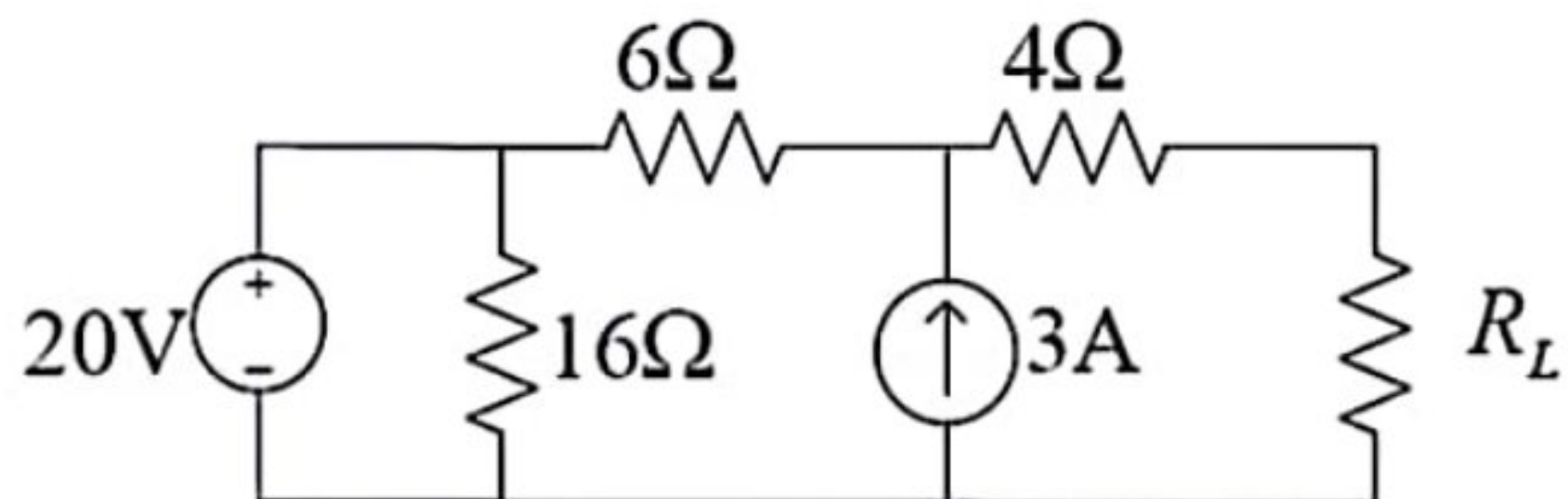5. Determine the value of R_L for maximum power transfer to the load of the following circuit. Calculate the maximum power. [CO2, Mark: 8]






EAST WEST UNIVERSITY
 Department of Computer Science and Engineering
 B.Sc. in Computer Science and Engineering Program
 Mid Term 2, Summer 2021


Course: CSE 109/209 – Electrical Circuits, Section-5
 Instructor: SHK, Senior Lecturer, CSE Department
 Full Marks: 40
 Time: 1 Hour and 30 Minutes [Including attachment time]

Note: There are FIVE questions, answer ALL of them. Course outcomes (CO), and marks of each question are mentioned at the right margin.

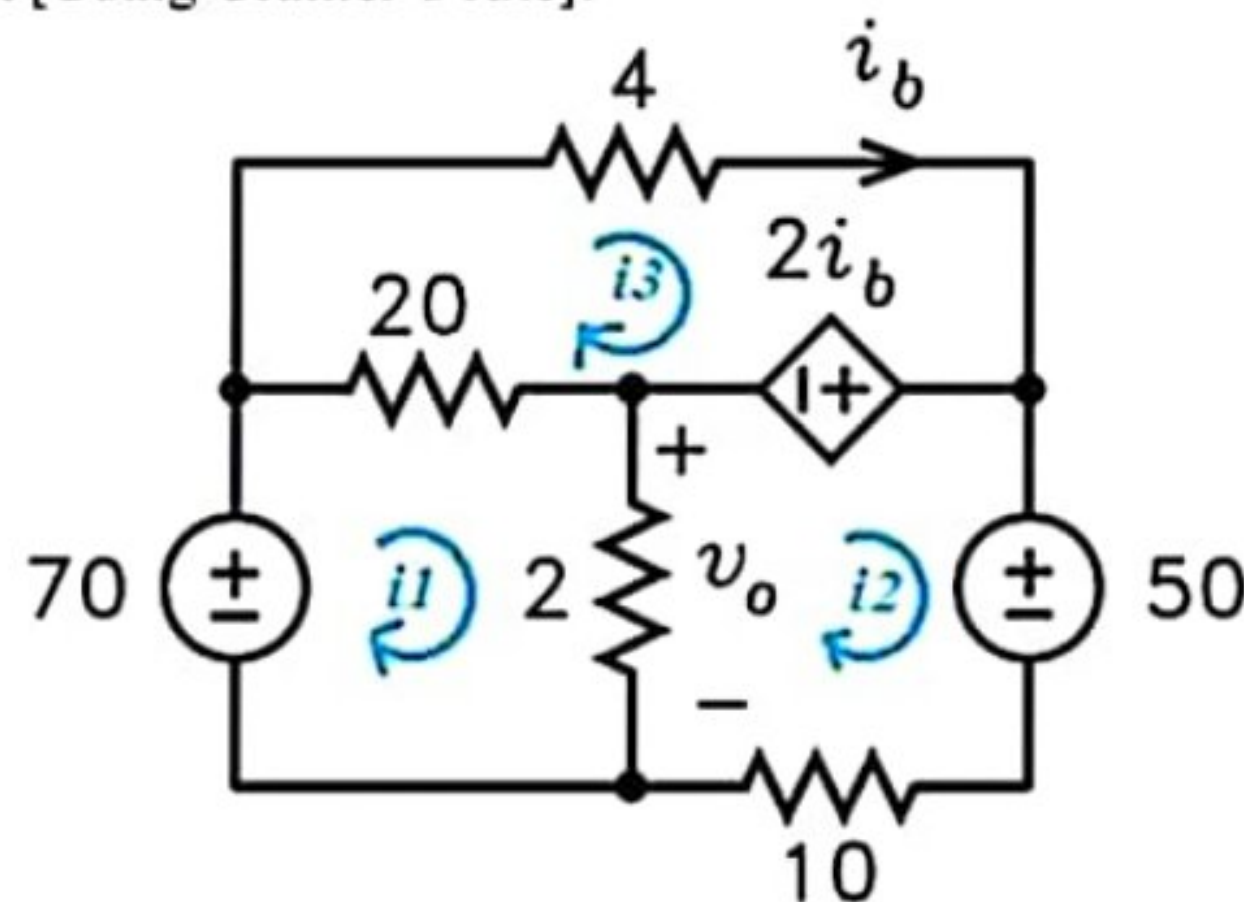
1. Using mesh currents indicated in the circuit, determine i_1 , i_2 and i_3 in the following circuit [Using Cramer's rule]. [CO2, Mark:12]



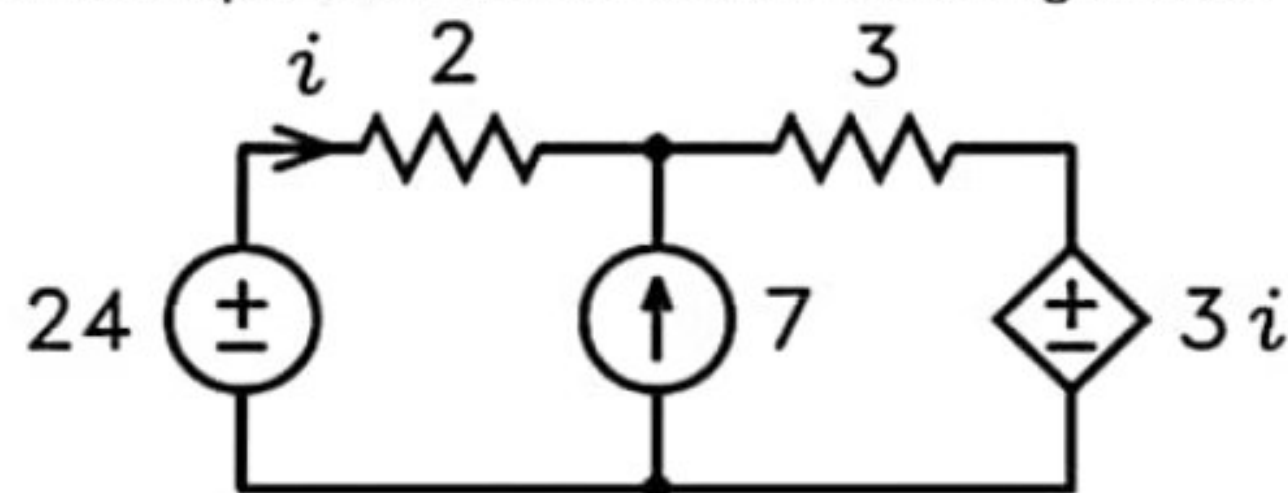
2. Use superposition technique to determine i in the following circuit. [CO2, Mark: 8]



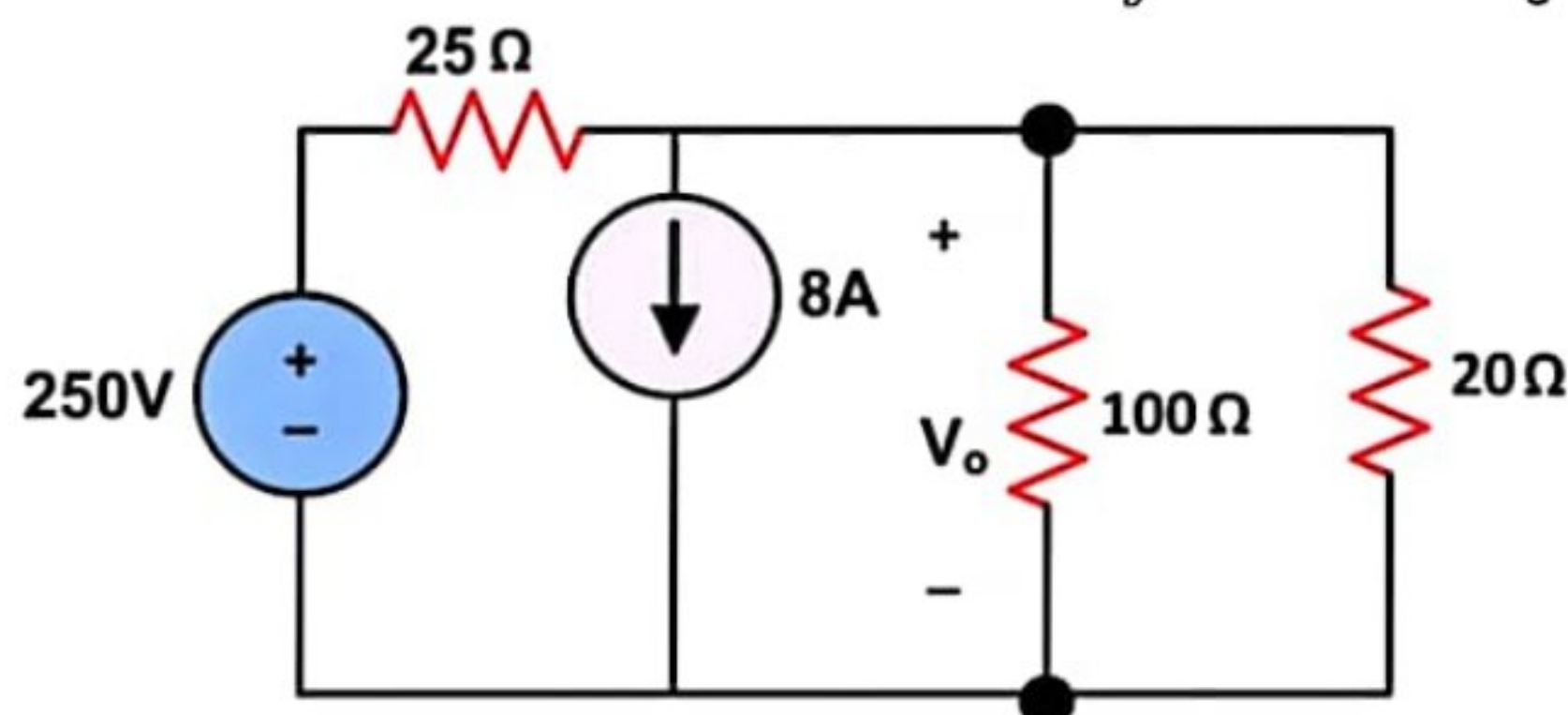
3. Use most effective source transformation to determine V_o in the following circuit. [CO2, Mark: 6]



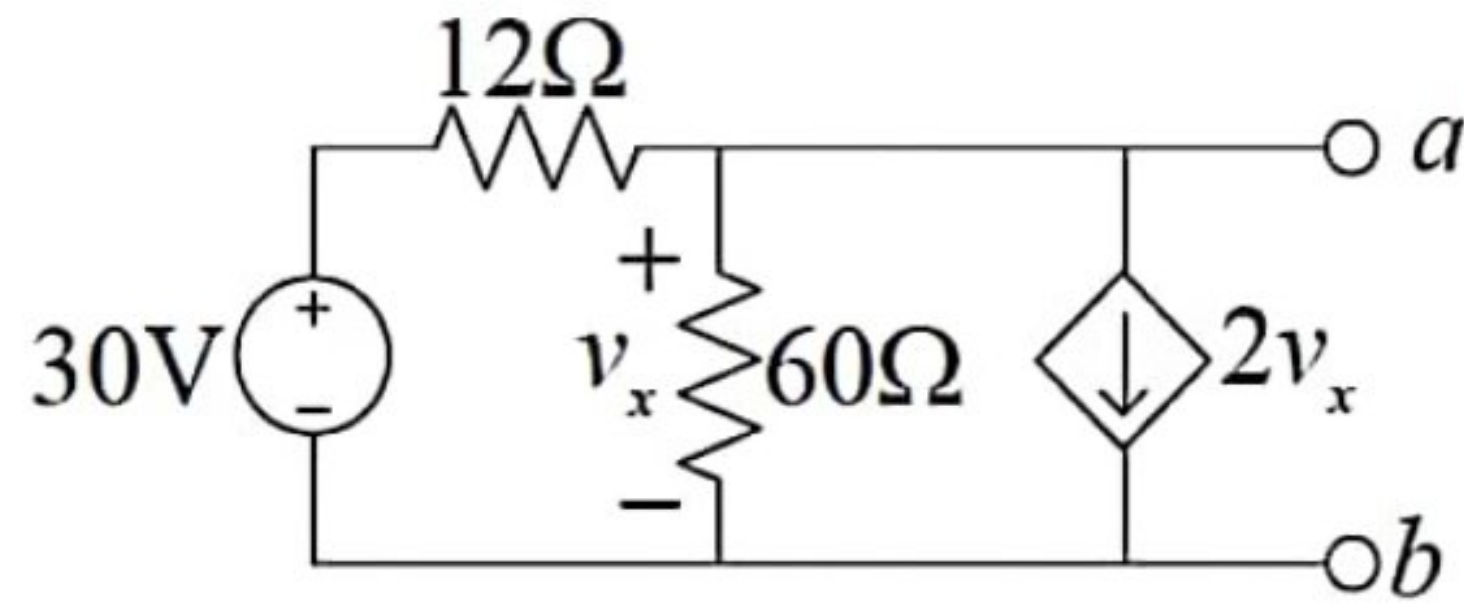4. Determine the Thevenin equivalent of the following circuit with respect to terminals a and b . [CO2, Mark:6]



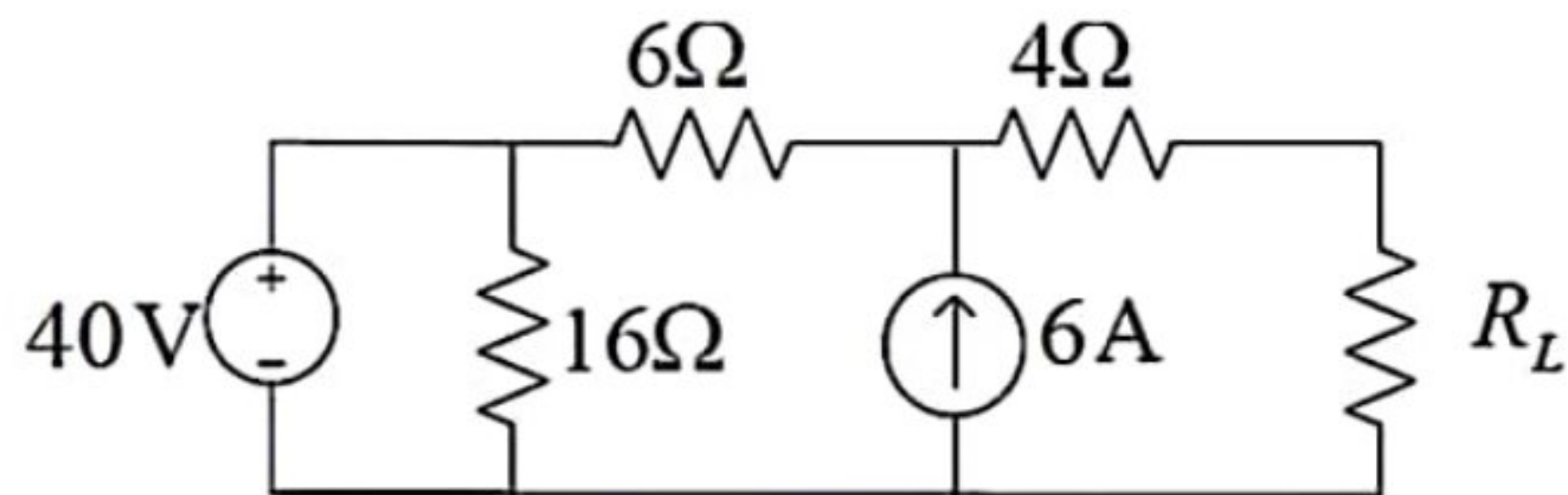5. Determine the value of R_L for maximum power transfer to the load of the following circuit. Calculate the maximum power. [CO2, Mark: 8]






EAST WEST UNIVERSITY
Department of Computer Science and Engineering
B.Sc. in Computer Science and Engineering Program
Mid Term 2, Fall 2021


Course: CSE 109/209 – Electrical Circuits, Section-5
Instructor: M. Saddam Hossain Khan, Senior Lecturer, CSE Department
Full Marks: 20
Time: 1 Hour and 30 Minutes [Including attachment time]

Note: There are FIVE questions, answer ALL of them. Course outcomes (CO), Cognitive level and marks of each question are mentioned at the right margin.

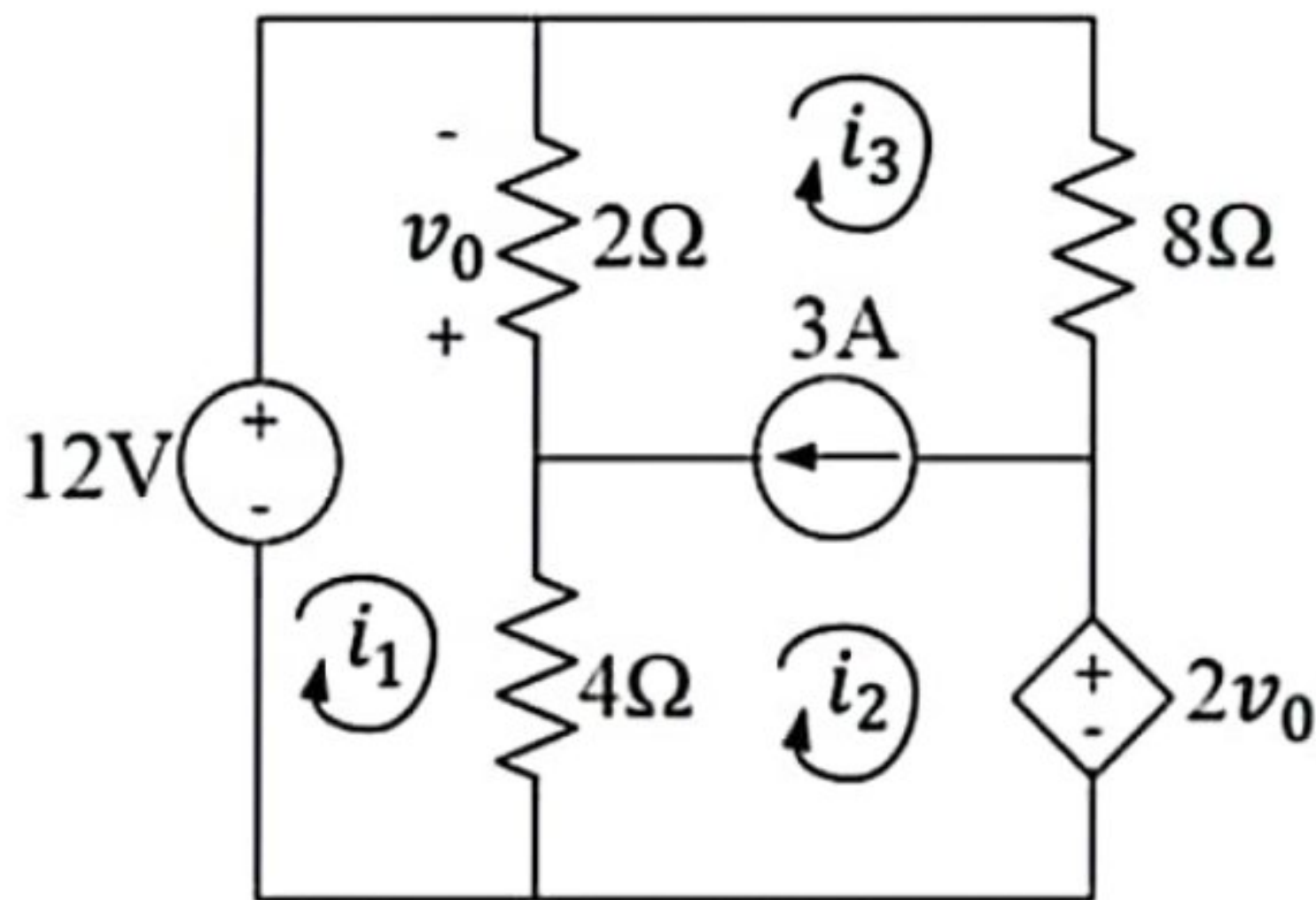
1. Using mesh currents indicated in the circuit, **determine** i_1 , i_2 and i_3 in the following circuit [Using Cramer's rule]. [CO2,C4, Mark: 6]



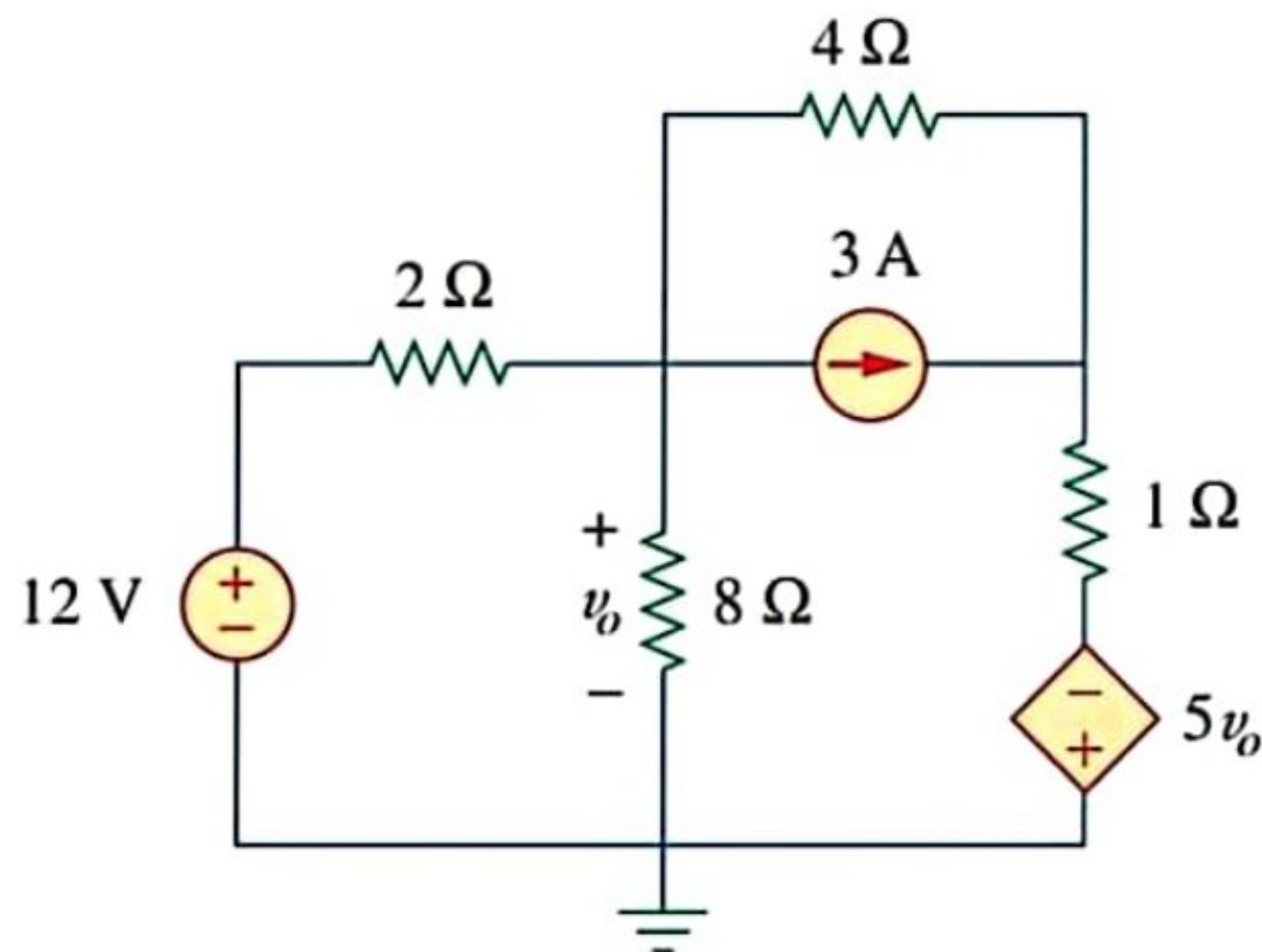
2. Use superposition technique to determine v_o in the following circuit. [CO2,C4, Mark: 4]



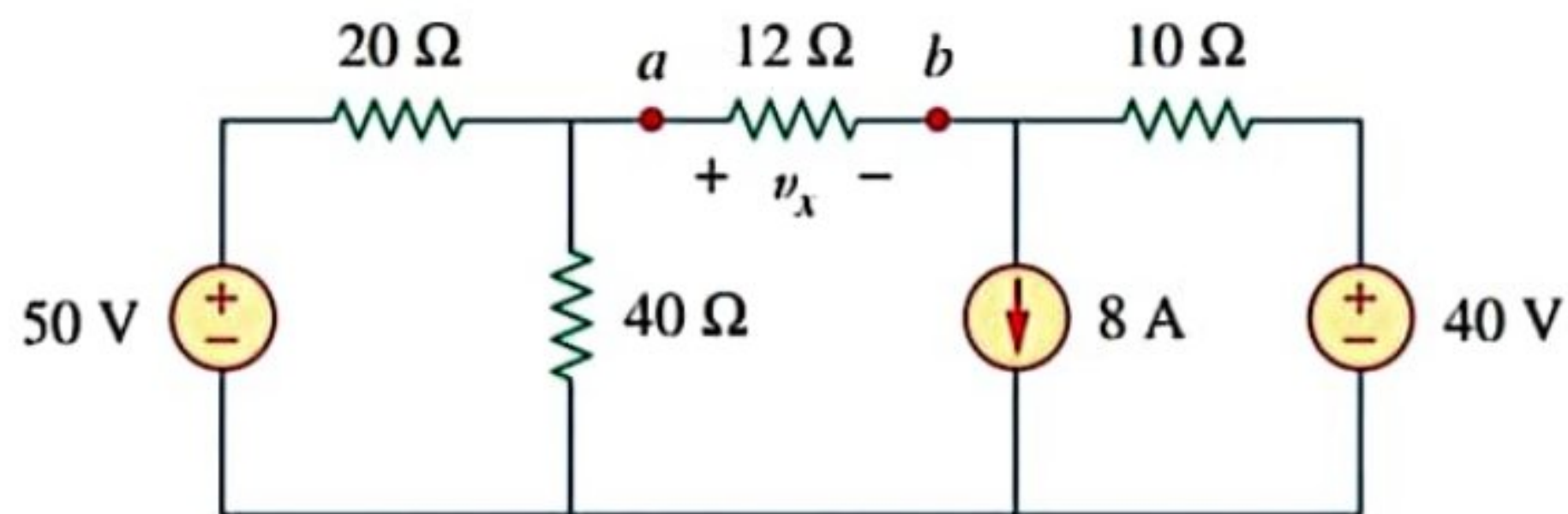
3. Use most effective source transformation to determine v_x in the following circuit. [CO2,C4, EP1, Mark: 3]



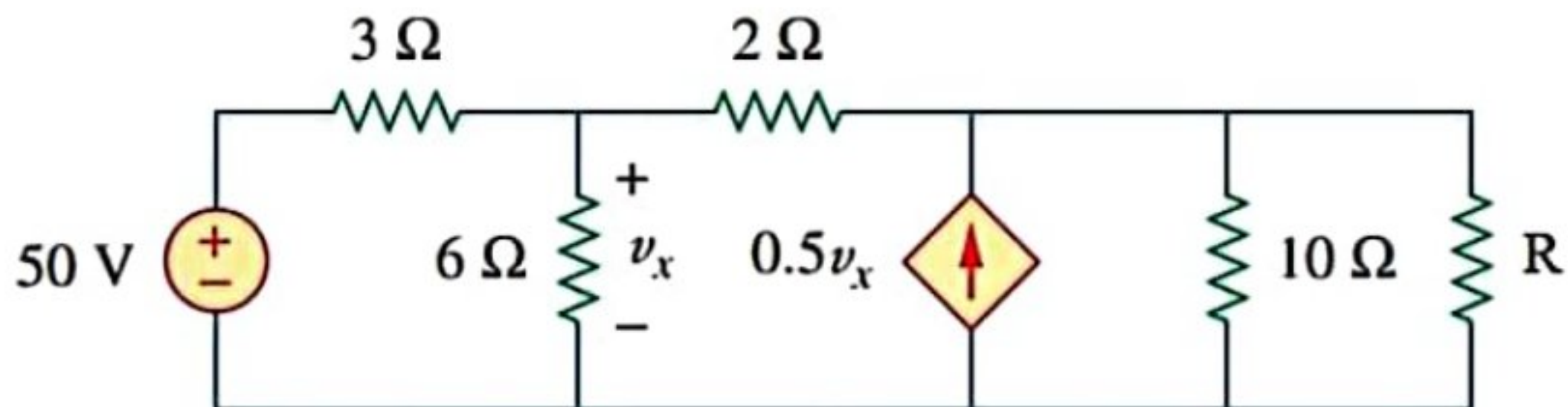4. Find the Thevenin's equivalent of the following circuit. Consider, the resistor R as the load. [CO2,C4, EP1,EP2, Mark: 4]



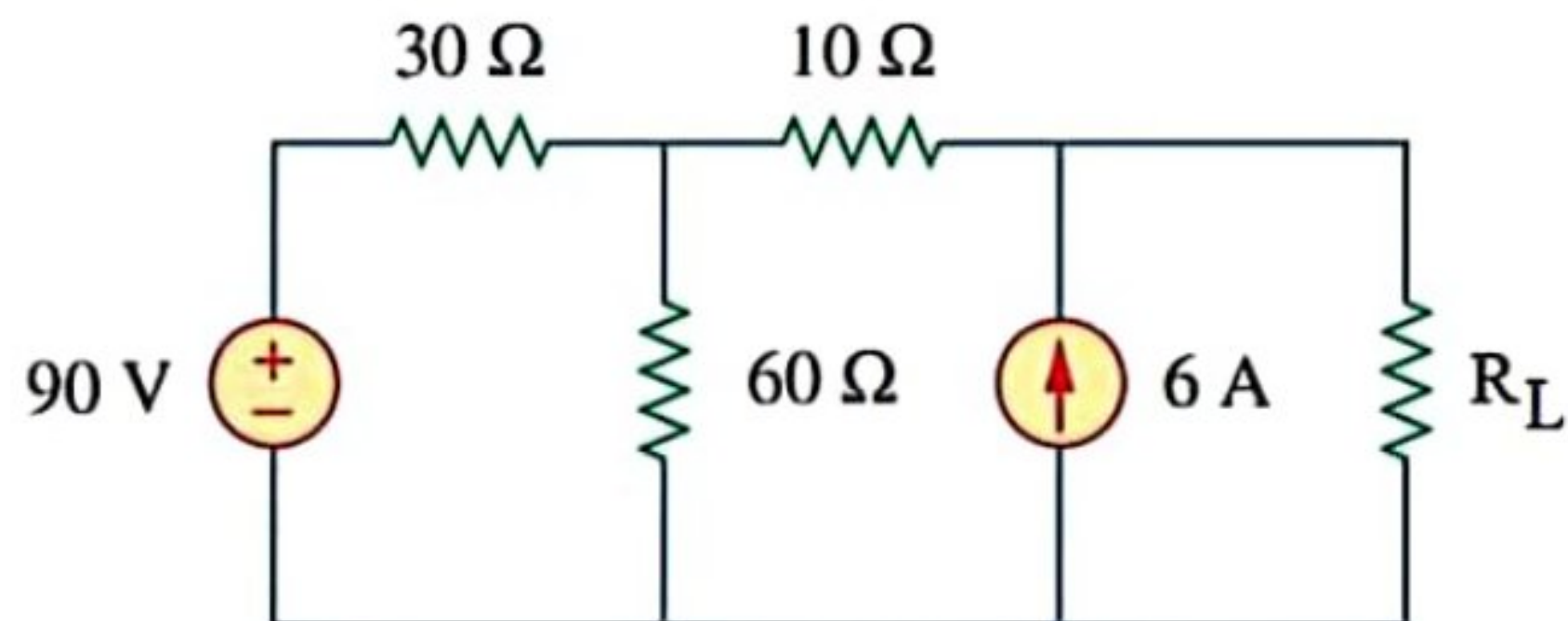5. Determine the value of R_L for maximum power transfer to the load of the following circuit. Calculate the maximum power. [CO2,C4, EP1,EP2, Mark: 3]






EAST WEST UNIVERSITY
Department of Computer Science and Engineering
B.Sc. in Computer Science and Engineering Program
Mid Term 2, Fall 2021


Course: CSE 109/209 – Electrical Circuits, Section-4
Instructor: M. Saddam Hossain Khan, Senior Lecturer, CSE Department
Full Marks: 20
Time: 1 Hour and 30 Minutes [Including attachment time]

Note: There are FIVE questions, answer ALL of them. Course outcomes (CO), Cognitive level and marks of each question are mentioned at the right margin.

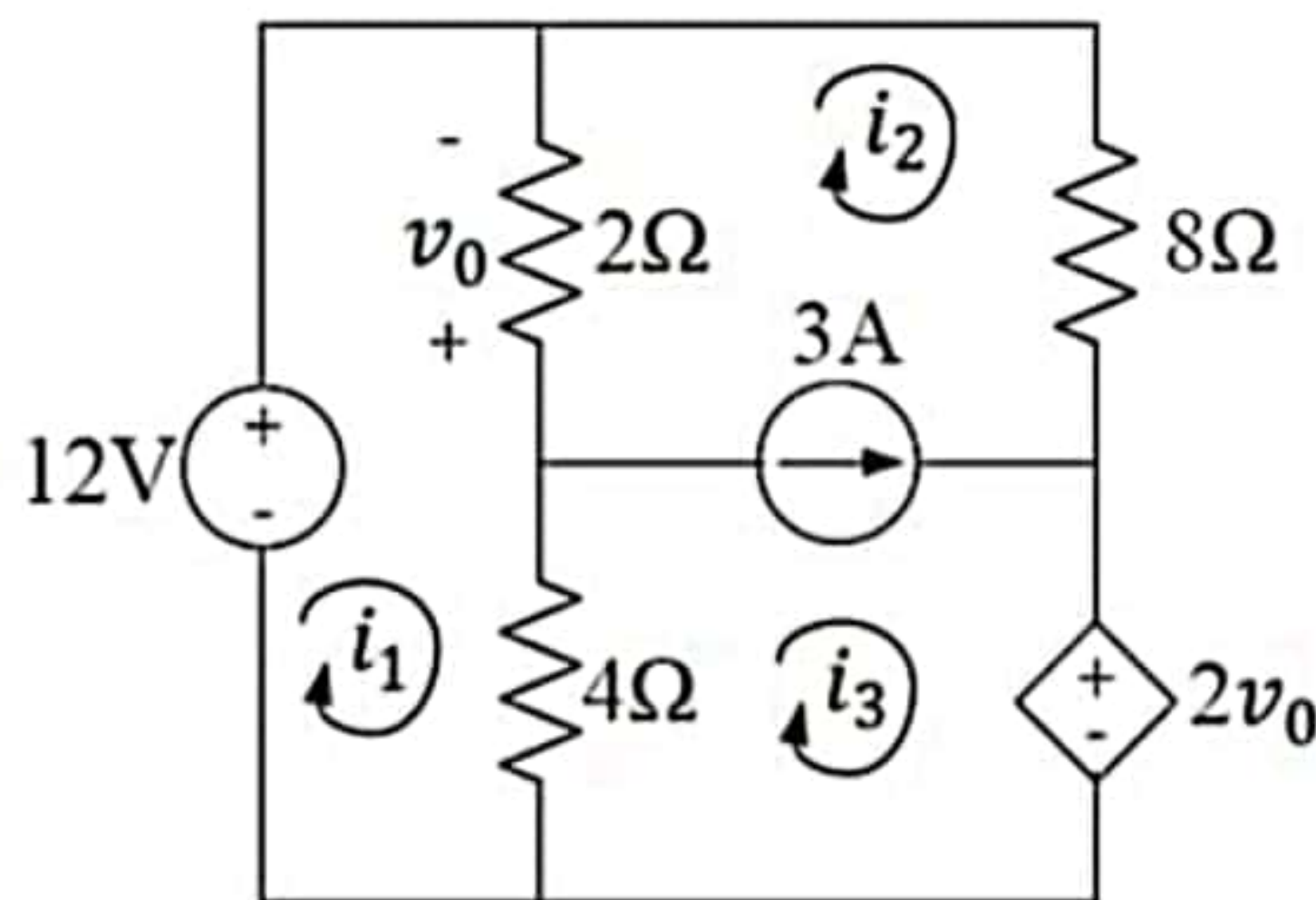
1. Using mesh currents indicated in the circuit, **determine i_1 , i_2 and i_3** in the following circuit [Using Cramer's rule]. [CO2,C4, Mark: 6]



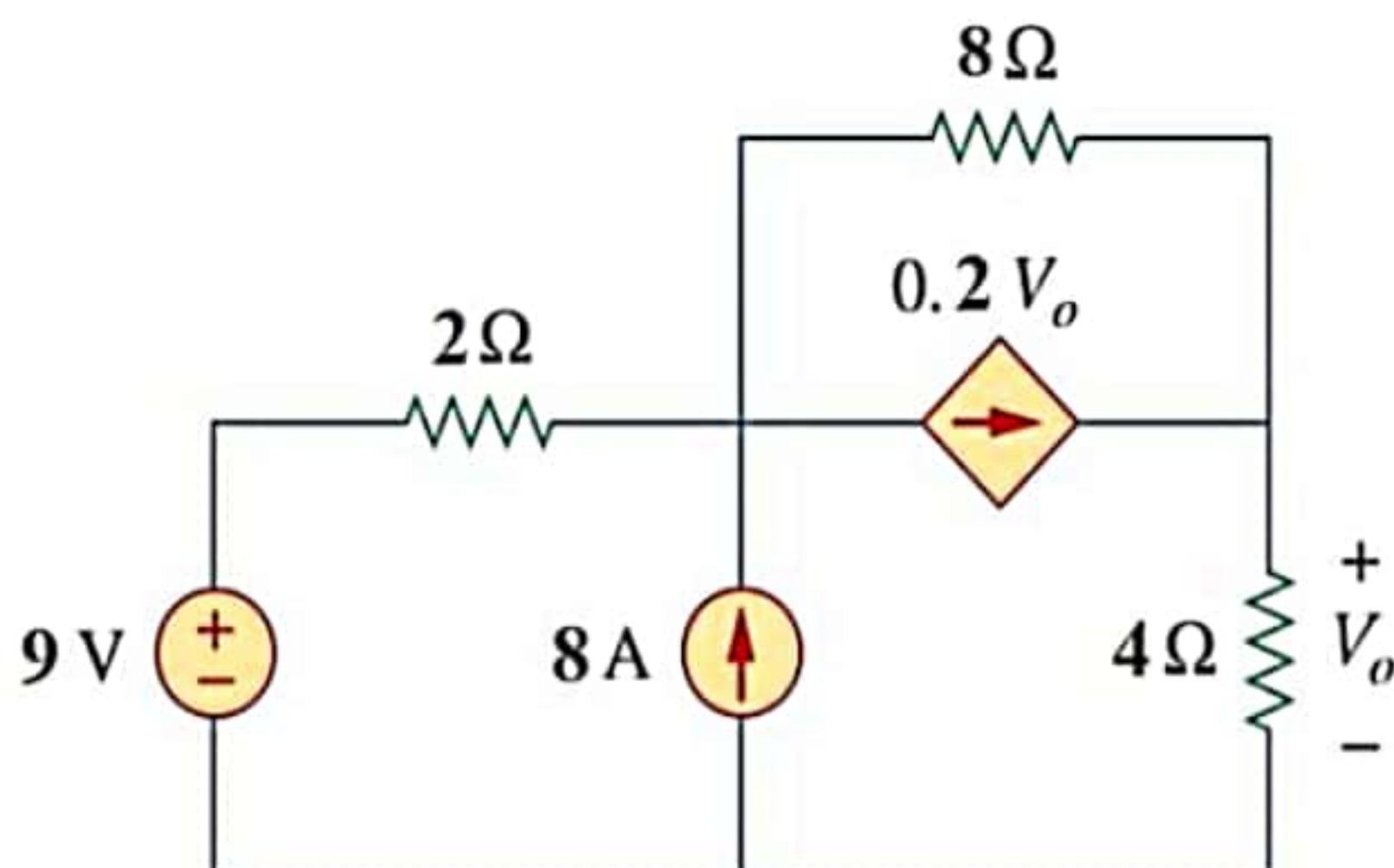
2. Use superposition technique to determine V_o in the following circuit. [CO2,C4, Mark: 4]



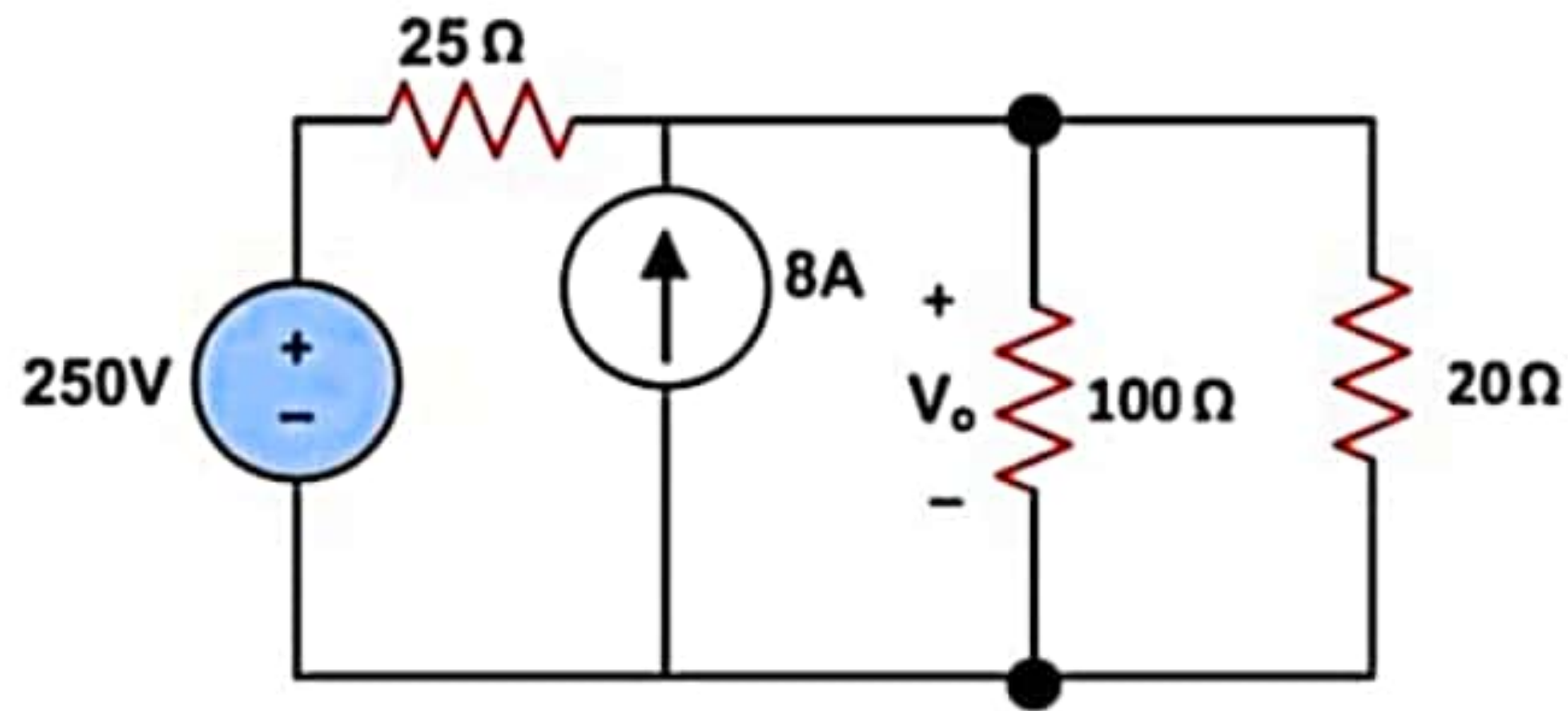
3. Use most effective source transformation to determine V_o in the following circuit. [CO2,C4, EP1, Mark: 3]



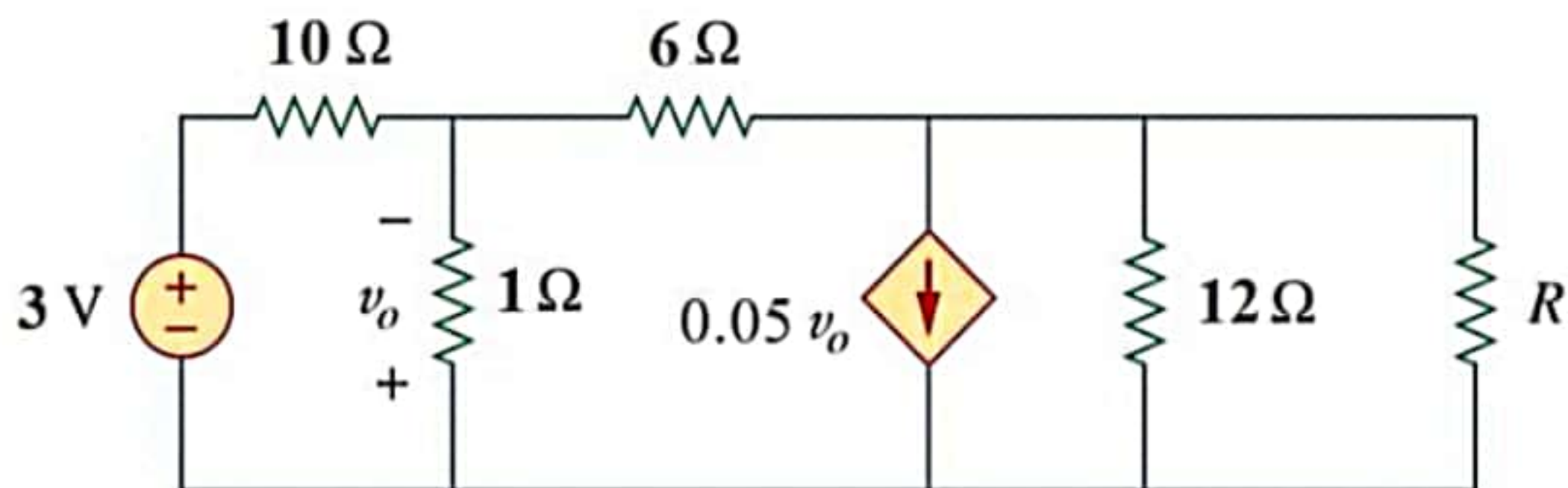4. Find the Norton's equivalent of the following circuit. Consider, the resistor R as the load. [CO2,C4, EP1,EP2, Mark: 4]



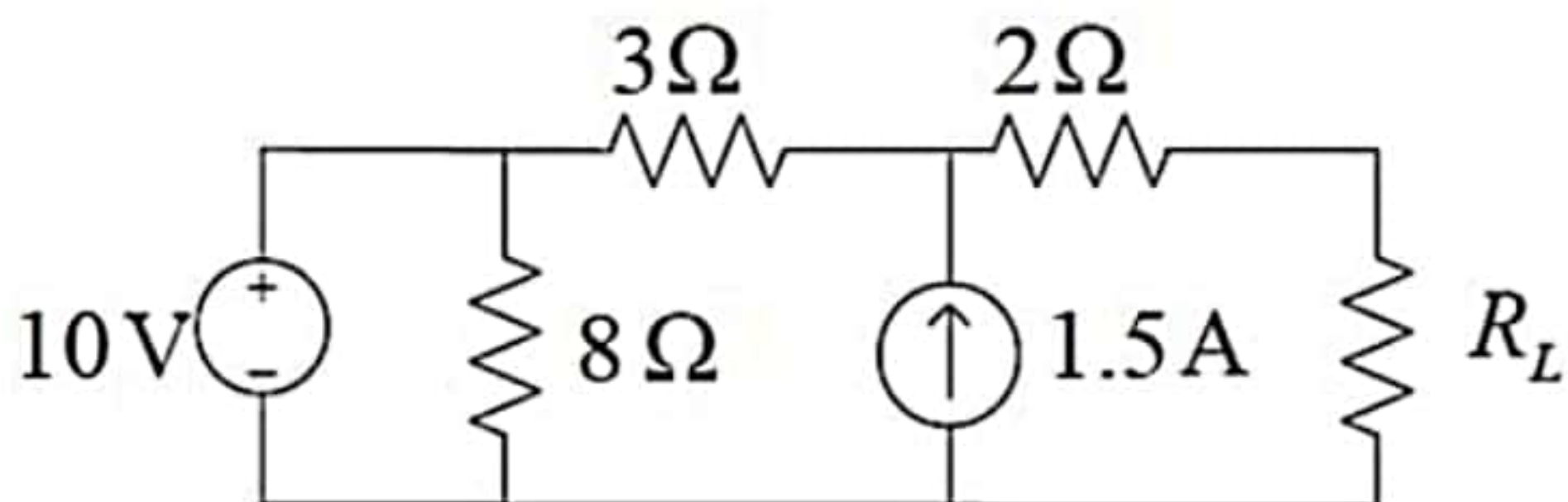5. Determine the value of R_L for maximum power transfer to the load of the following circuit. Calculate the maximum power. [CO2,C4, EP1,EP2, Mark: 3]






EAST WEST UNIVERSITY
Department of Computer Science and Engineering
B.Sc. in Computer Science and Engineering Program
In Course Assessment - 2, Spring 2021

Course: CSE 209 – Electrical Circuits, Section-4
Instructor: SHK, Senior Lecturer, CSE Department
Full Marks: 19
Time: 1 Hour and 30 Minutes [Including submission time]

Note: There are FOUR questions, answer ALL of them. Course outcomes (CO), cognitive levels and marks of each question are mentioned at the right margin.


1a. Apply nodal analysis to determine i_0 from the circuit given below.

[CO2,
Mark:4]

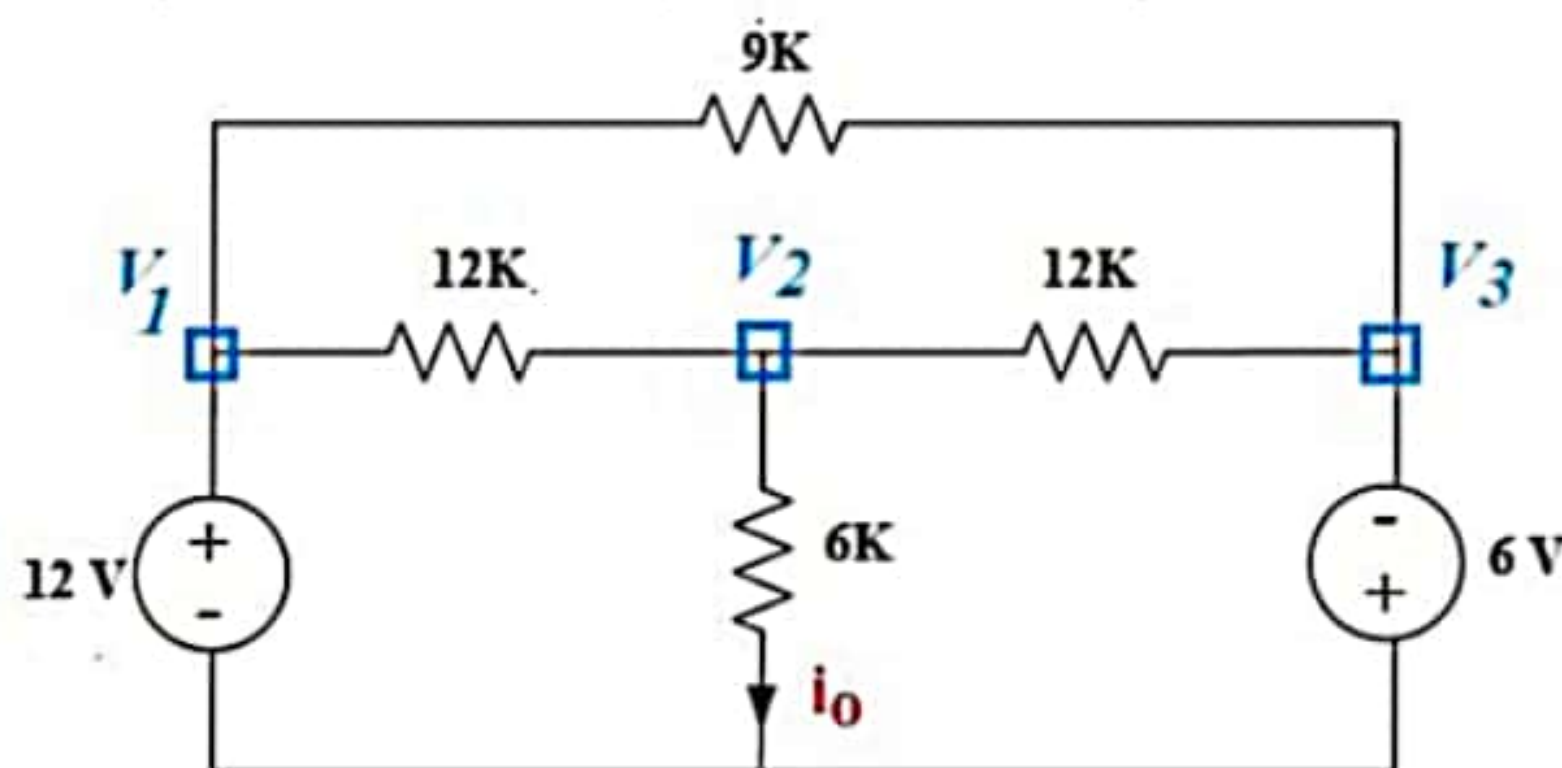


1b. Using nodal analysis, determine V_X from the circuit given below.

[CO2,
Mark:2]

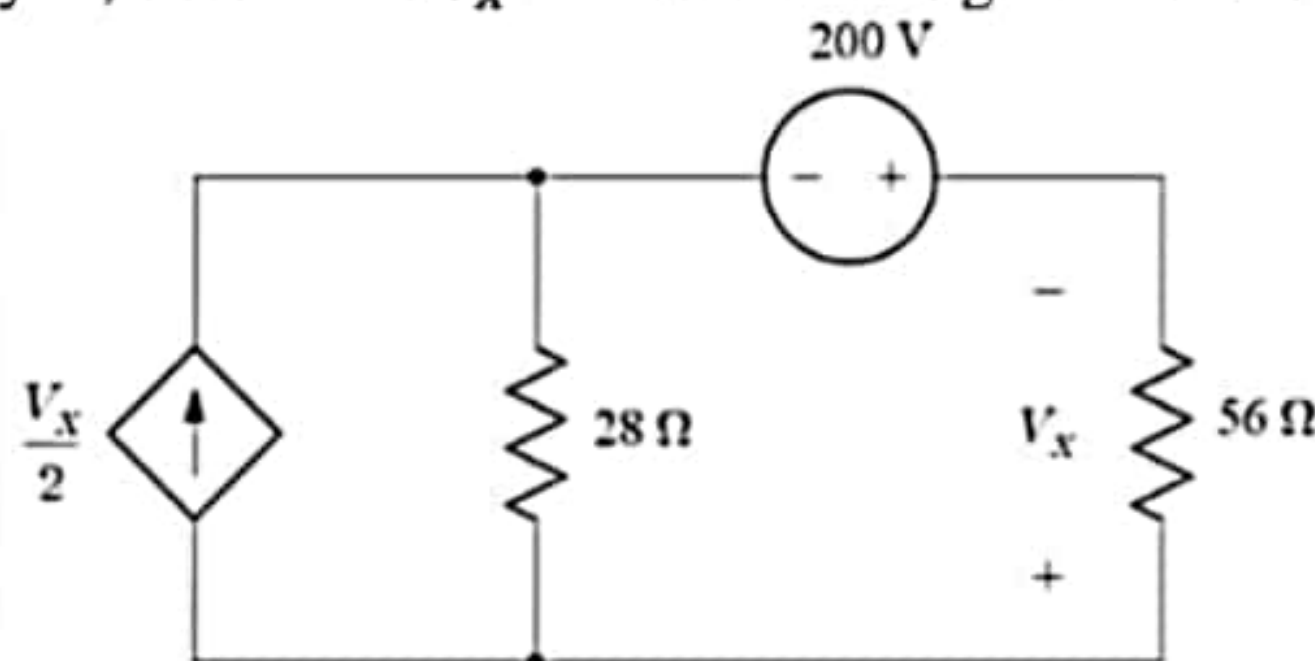


2. Using mesh currents indicated in the circuit, determine v_0 in the following circuit.

[CO2,
Mark:6]

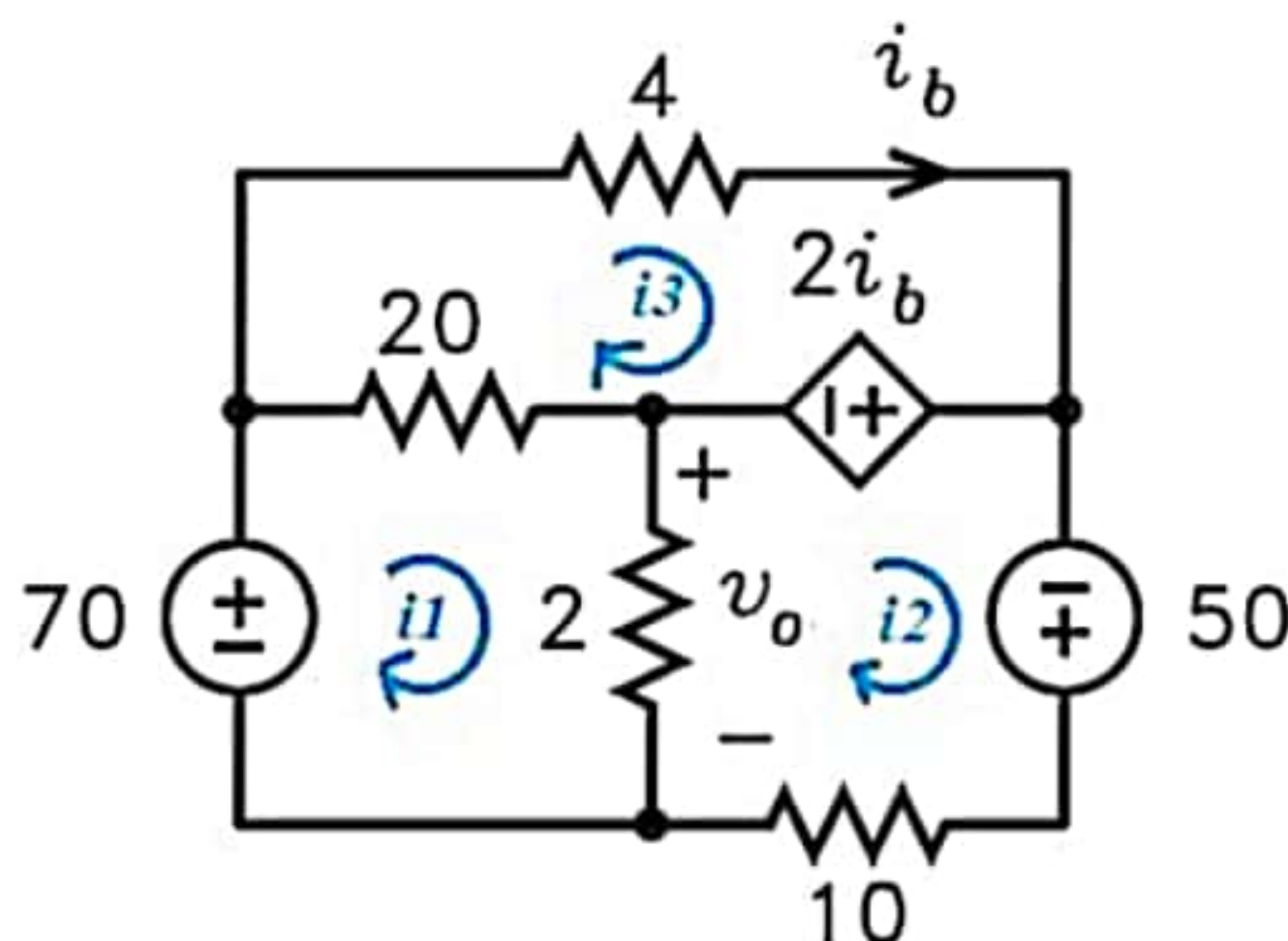

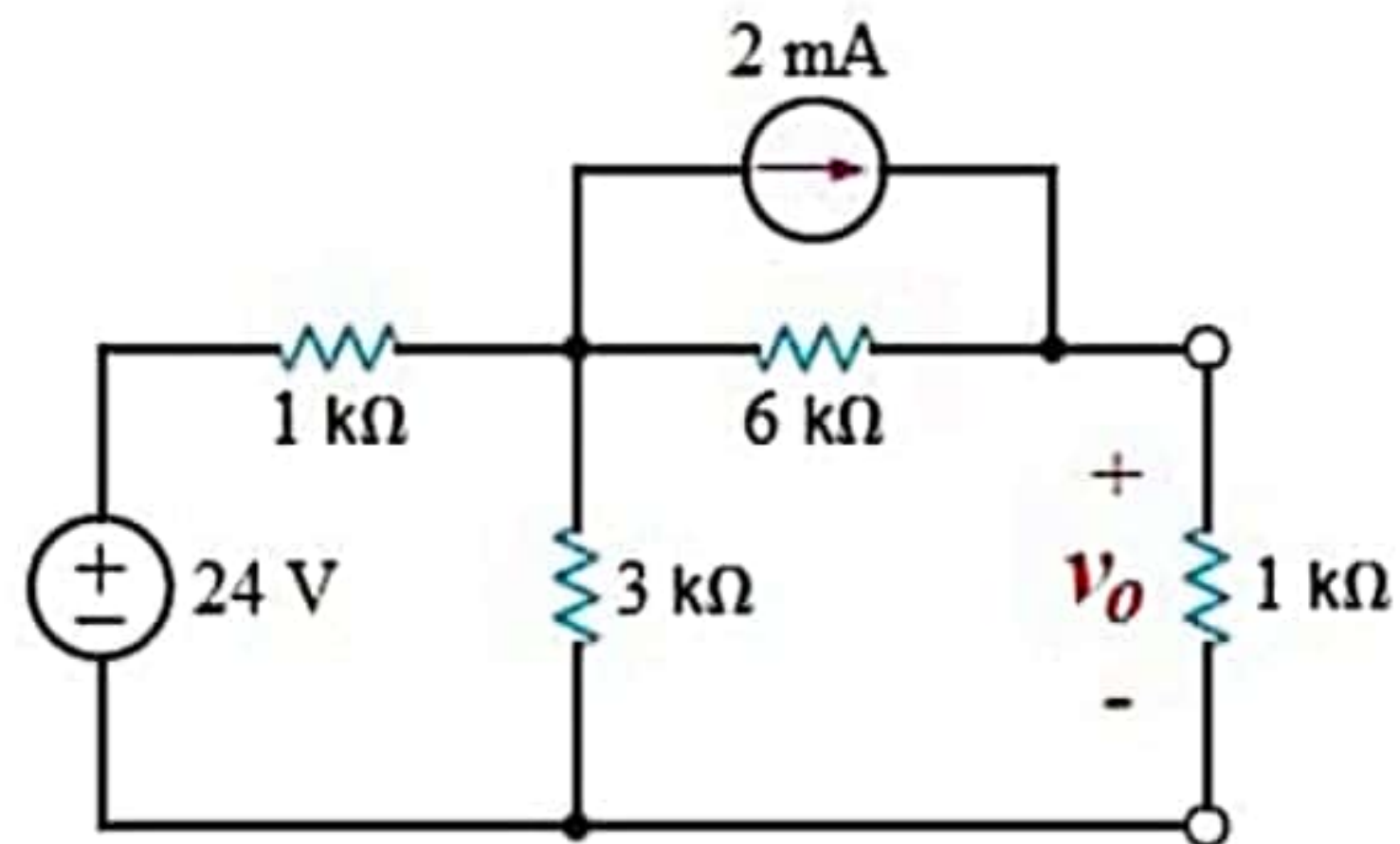3. Use most effective source transformation to determine v_o in the following circuit. [CO2, Mark: 3]



4. Use superposition technique to determine i in the following circuit. [CO2, Mark: 4]

