

Fundamentals of Electric Circuits

By
Alexander-Sadiku

Chapter 1

Basic Concepts

Basic Concepts - Chapter 1

- Electric Circuit.
- Systems of Units.
- Electric Charge.
- Current.
- Voltage.
- Power and Energy.
- Circuit Elements.

Electrical Circuit


- An electric circuit is an interconnection of electrical elements.

A Basic Circuit

All electric circuits have three main parts

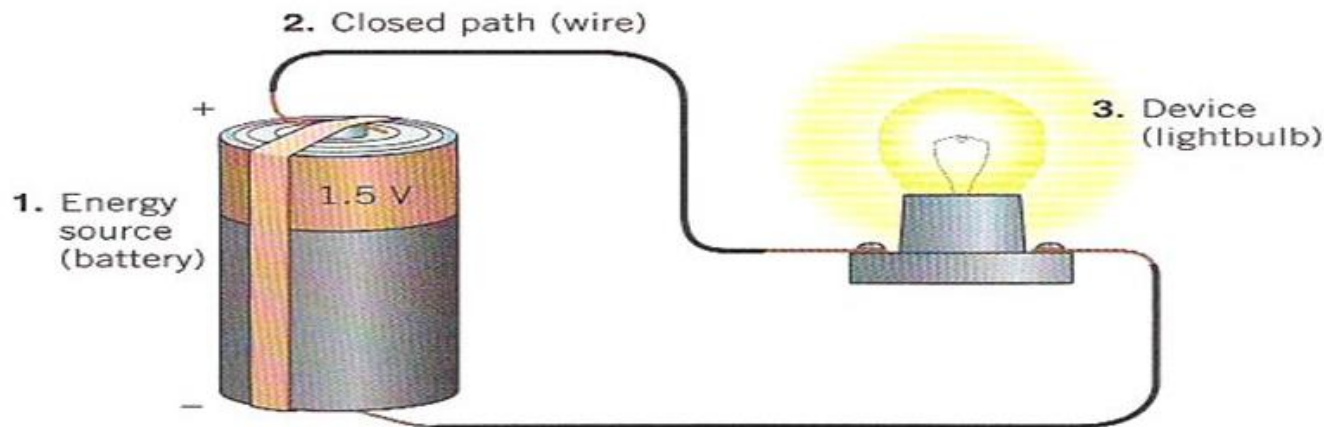1. A source of energy
2. A closed path
3. A device which uses the energy

If ANY part of the circuit is open the device will not work!



System of Units (1)

Six basic units

| Quantity | Basic unit | Symbol |
|----------------------------------|-------------------|---------------|
| Length | meter | m |
| Mass | kilogram | Kg |
| Time | second | s |
| Electric current | ampere | A |
| Thermodynamic temperature | kelvin | K |
| Luminous intensity | candela | cd |

System of Units (2)

The derived units commonly used in electric circuit theory

| Quantity | Unit | Symbol |
|-----------------------|---------|----------|
| electric charge | coulomb | C |
| electric potential | volt | V |
| resistance | ohm | Ω |
| conductance | siemens | S |
| inductance | henry | H |
| capacitance | farad | F |
| frequency | hertz | Hz |
| force | newton | N |
| energy, work | joule | J |
| power | watt | W |
| magnetic flux | weber | Wb |
| magnetic flux density | tesla | T |

| Factor | Prefix | Symbol |
|------------|--------|--------|
| 10^9 | giga | G |
| 10^6 | mega | M |
| 10^3 | kilo | k |
| 10^{-2} | centi | c |
| 10^{-3} | milli | m |
| 10^{-6} | micro | μ |
| 10^{-9} | nano | n |
| 10^{-12} | pico | p |

Decimal multiples and
submultiples of SI units

Electric Charges


- **Charge** is an electrical property of the atomic particles of which matter consists, measured in **coulombs (C)**.
- The charge **e** on one electron is negative and equal in magnitude to **1.602×10^{-19} C** which is called as electronic charge. The charges that occur in nature are **integral multiples** of the electronic charge.
- Law of conservation of charge
- Mobility

Current (1)

- Electric current $i = dq/dt$. The unit of ampere can be derived as $1 \text{ A} = 1\text{C/s}$.
- A **direct current (dc)** is a current that remains constant with time.
- An **alternating current (ac)** is a current that varies sinusoidally with time. (reverse direction)


Current (2)

- The direction of current flow

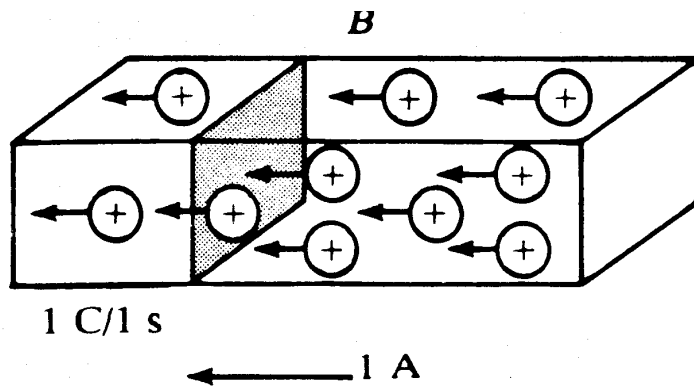

(a)

Positive ions

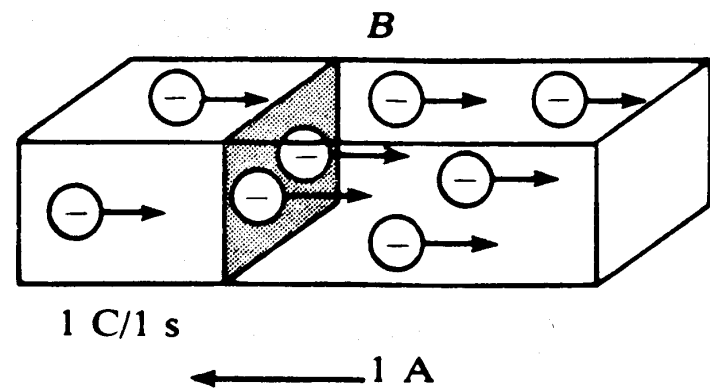

(b)

Negative ions

Voltage


- Voltage (or potential difference) is the **energy** required to move a **unit charge** through an element, measured in volts (V).
- Mathematically,
$$v_{ab} = dw / dq$$
 (volt)
 - **w** is energy in joules (J) and **q** is charge in coulomb (C).
- Electric voltage, v_{ab} , is always **across the circuit element** or **between two points in a circuit**.
 - $v_{ab} > 0$ means the potential of **a** is higher than potential of **b**.
 - $v_{ab} < 0$ means the potential of **a** is lower than potential of **b**.

Power and Energy (1)


- Power is the time rate of expending or absorbing energy, measured in watts (W).

- Mathematical expression:
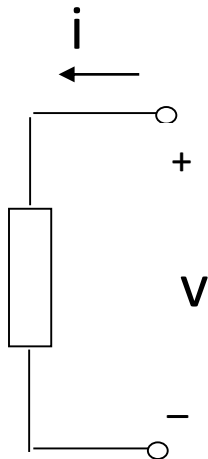
$$p = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt} = vi$$



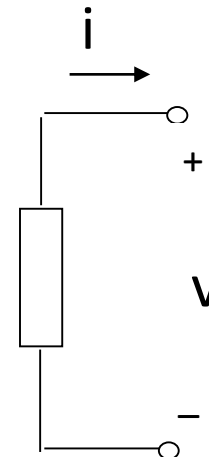Passive sign convention
 $P = +vi$
absorbing power



$p = -vi$
supplying power

Power and Energy (2)

- The law of conservation of energy


$$\sum p = 0$$

- Energy is the capacity to do work, measured in joules (J).
- Mathematical expression $w = \int_{t_0}^t p dt = \int_{t_0}^t v i dt$


Circuit Elements (1)

Active Elements

Passive Elements

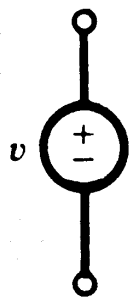

(a)

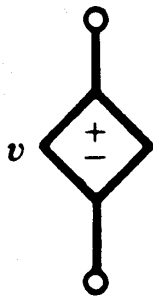

(b)



(c)



(d)




(e)



(f)



(g)

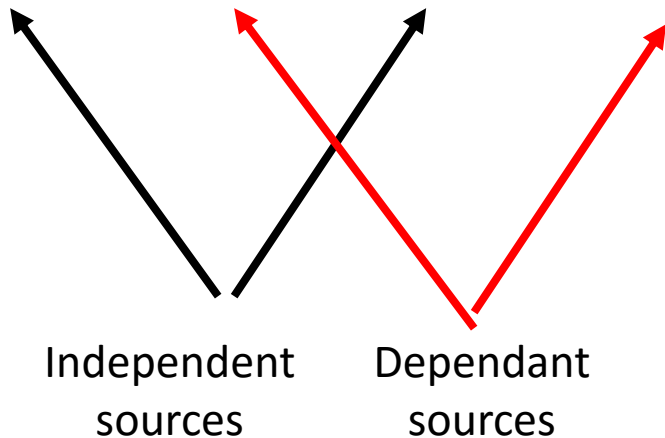

- A dependent source is an active element in which the source quantity is controlled by another voltage or current.
- They have four different types: VCVS, CCVS, VCCS, CCCS. Keep in mind the signs of dependent sources.

Circuit Elements (2)

Example 2

Obtain the voltage v in the branch shown in Figure 2.1.1P for $i_2 = 1\text{A}$.

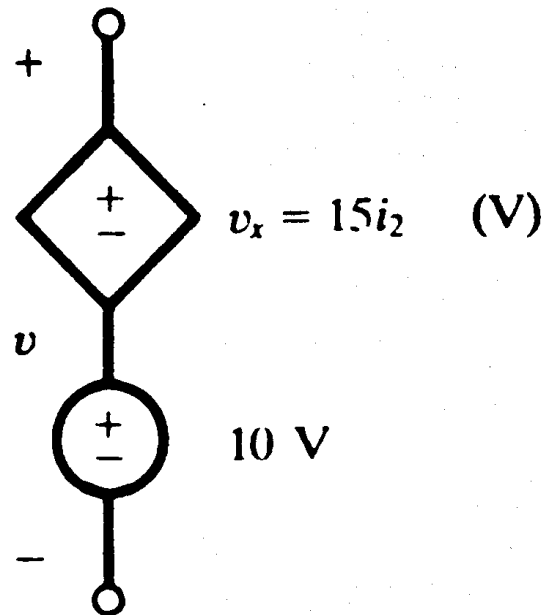


Figure 2.1.1P

Circuit Elements (3)

Solution

Voltage v is the sum of the current-independent 10-V source and the current-dependent voltage source v_x .

Note that the factor 15 multiplying the control current carries the units Ω .

Therefore, $v = 10 + v_x = 10 + 15(1) = 25 \text{ V}$