



**EAST WEST UNIVERSITY**  
**Department of Computer Science and Engineering**  
**B.Sc. in Computer Science and Engineering Program**  
**Final Examination, Summer 2021 Semester**

**Course:** CSE 109/209 Electrical Circuits, Section-5  
**Instructor:** M. Saddam Hossain Khan, Senior Lecturer, CSE Department  
**Full Marks:** 20 (20 will be counted for final grading)  
**Time:** 1 Hour and 30 Minutes (Including submission)

**Note:** There are FIVE questions, answer ALL of them. Course Outcome (CO), Cognitive Level and Mark of each question are mentioned at the right margin.

1. Determine  $v(t)$  and  $i(t)$  in the following circuit.

[CO1,C2,  
Mark:3]


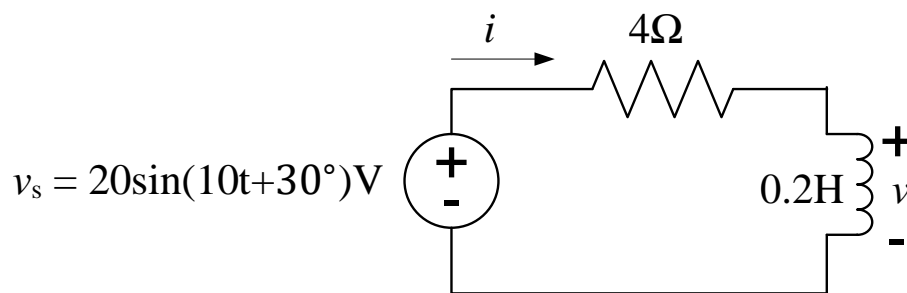


Figure 1


2. Determine  $Z_{eq}$  and  $I$  for the following circuit.

[CO1,C2,  
Mark: 3]

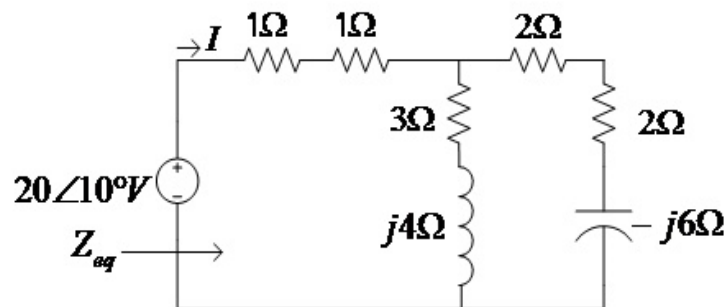


3. Using nodal analysis, compute  $v_2(t)$  for the following circuit [Show analysis using Cramer's rule].

[CO3,C4,  
Mark: 4]

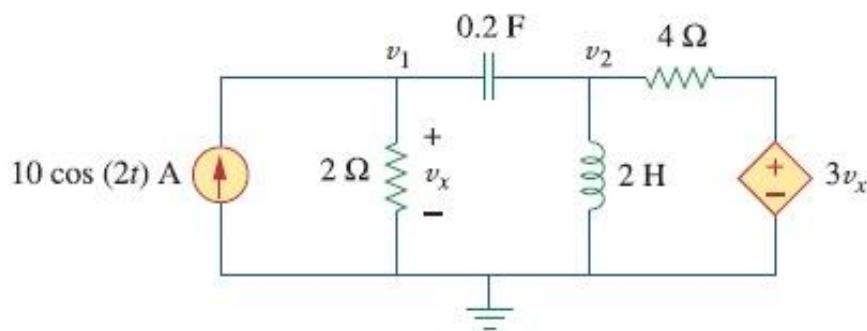


4. Using the superposition principle, **find**  $V_x$  in the following circuit.

[CO3,C4,  
Mark:4]

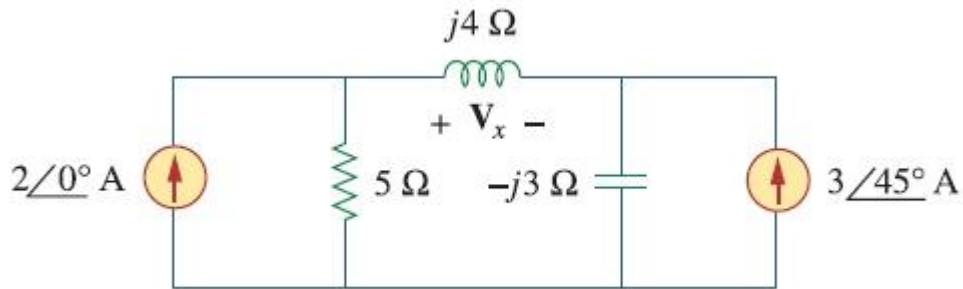

5. a) **Find** the value of  $Z_L$  that will absorb the maximum power and the value of the maximum power in the following circuit.

[CO3,C4,  
Mark:6]

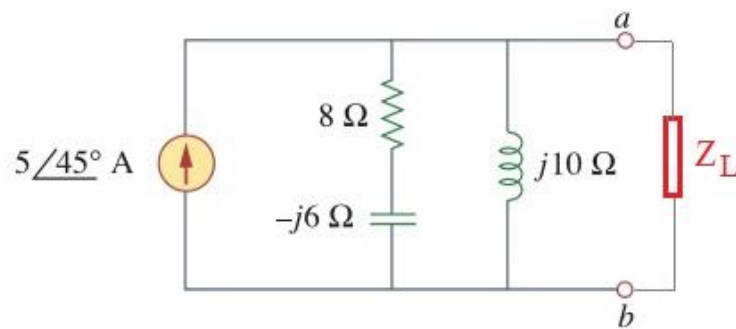

- b) **Find** the average power supplied by the source and absorbed by the resistor from Figure 1.