

Course: CSE209 Electrical Circuits

Expt No.: 7

Title: DC Circuit Analysis in PSpice using Source and Resistance Sweep

Objectives:

1. To analyze DC circuit in PSpice by sweeping source and resistance.
2. To verify maximum power transfer theorem.

Introduction:

In PSpice, DC analysis may be performed by varying the value of a DC voltage source or by varying a resistance. The results of such sweeps may be graphically viewed using the Probe tool of PSpice.

Circuit Diagram:

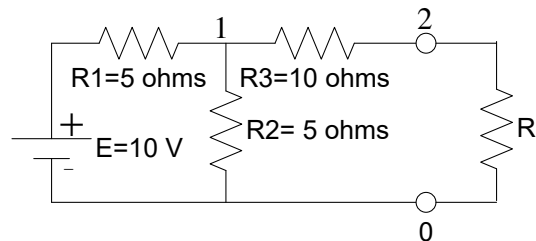


Figure 1. Example circuit.

Pre-Lab Report Question:

1. Theoretically calculate the value of R_L for maximum power transfer in the circuit of Figure 1.
2. Theoretically calculate the node voltages $V(1)$ and $V(2)$ in the circuit of Figure 1. Also calculate the current $I(R3)$ passing through the resistance $R3$.

Lab Procedure:

1. Draw the circuit of Figure 1 (except the load resistance R_L) in Schematics and simulate the circuit to determine the open circuit voltage V_{oc} between nodes 2 and 0. For this purpose, connect a 0A current source between nodes 2 and 0.
2. Remove the 0A current source from nodes 2 and 0. Connect a 0V voltage source between nodes 2 and 0. Simulate the circuit to determine the short circuit current I_{sc} flowing from node 2 to node 0.
3. Calculate $E_{th} = V_{oc}$ and $R_{th} = V_{oc} / I_{sc}$ from the simulations performed in steps 1 and 2. $R_L = R_{th}$ for maximum power transfer
4. Remove the 0V voltage source from nodes 2 and 0. Connect a 10 Ohm resistance R_L between nodes 2 and 0. In the *Analysis Setup* dialog box, click the *DC Sweep* button. Select *Linear* type and *Voltage source* as a sweep variable. Write E as a sweep variable name with *Start value* = 0V, *End value* = 20V and *Increment* = 1V. Simulate the circuit. If simulation is successfully completed, a *Probe* window will appear with E being the x-axis. Click *Add Trace* in Probe window and select $V(1)$ and $V(2)$. Add another plot to the window and add $I(R3)$. From the plots using the cursor, determine the values of $V(1)$, $V(2)$ and $I(R3)$ at $E = 10V$.

5. Now, vary the resistance R_L and observe circuit variables as functions of R_L .
 - a. Double-click on the value label of the resistor R_L , which is to be varied. This will open a *Set Attribute Value* dialog box. Enter the name **{RVAR}** (including the curly braces) in place of the component value.
 - b. Choose *Get New Part* from the menu and select the part named *param*. Place the box anywhere on the schematic page. Double-click on the word *PARAMETERS* in the box title to bring up the parameter dialog box. Set the *NAME1*= **RVAR** (without the curly braces), which is the same name given to the resistor to be varied, and the *VALUE1*= 10 (or any other arbitrary value).
 - c. In the *Analysis Setup* dialog box, click the *DC Sweep* button and select *Linear* type and *Global Parameter* as a sweep variable. Type **RVAR** as a sweep variable *Name* with *Start value* = 1, *End value* = 20 and *Increment* = 0.1. Simulate the circuit and if simulation is successful, a Probe window will appear.
 - d. From the plots, determine $V(1)$, $V(2)$ and $I(R3)$ for $R = 10$ ohm.
 - e. Delete the existing plots and select $I(R3)*I(R3)*RVAR$ for plot as a function of load resistance. Note that $I(R3)*I(R3)*RVAR$ represents the load power. Determine the maximum value of the load power and the value of load resistance R_L for which the load power is the maximum. How does this value compare with R_{th} of the circuit?
6. Take printouts of the simulated circuits corresponding to steps 1 and 2. Also take printouts of the Probe plots corresponding to steps 4 and 5. Have the printouts signed by the instructor.

Post-Lab Report Questions:

1. Compare the values of $V(1)$, $V(2)$ and $I(R3)$ obtained in steps 4 and 5(d).
2. Compare the load resistance R_L for maximum power transfer obtained in steps 2 and 5(e).
3. Compare the theoretical solutions with the solutions obtained from PSpice and comment on any observed discrepancy.