



# EAST WEST UNIVERSITY

Department of Computer Science and Engineering


B.Sc. in Computer Science and Engineering Program

Final Examination, Fall 2021 Semester


**Course:** CSE 109/209 Electrical Circuits, Section-5  
**Instructor:** M. Saddam Hossain Khan, Senior Lecturer, CSE Department  
**Full Marks:** 20 (20 will be counted for final grading)  
**Time:** 1 Hour and 30 Minutes (Including submission)

**Note:** There are FIVE questions, answer ALL of them. Course Outcome (CO), Cognitive Level and Mark of each question are mentioned at the right margin.

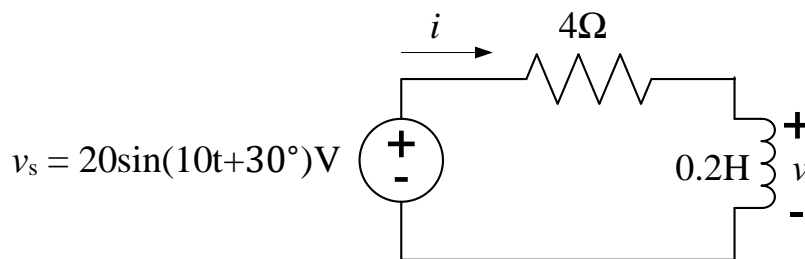
1. **Determine**  $v(t)$  in the following circuit. Also, **find** the average power supplied by the source and absorbed by the resistor. [CO1, C2, Mark:3]



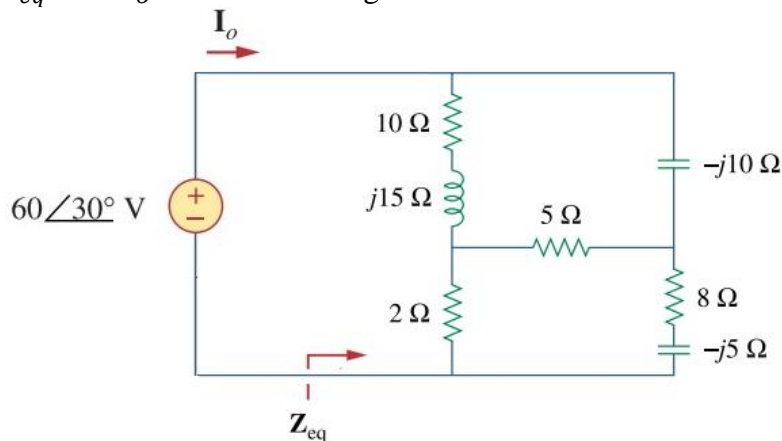2. **Determine**  $Z_{eq}$  and  $I_o$  in the following circuit. [CO1, C2, Mark: 3]




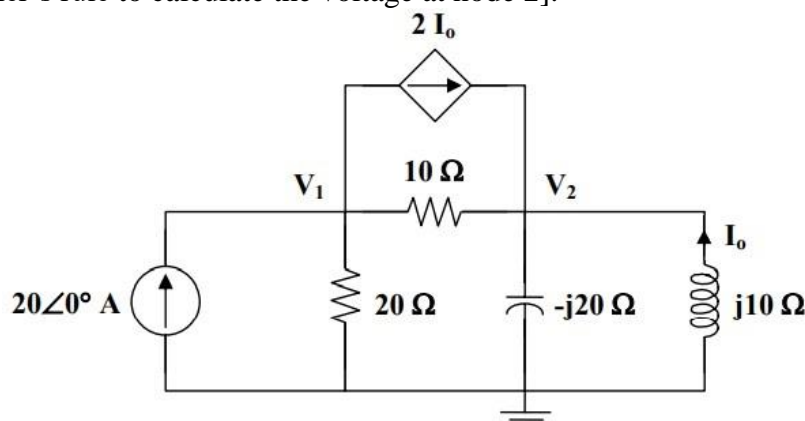3. Using nodal analysis, **compute**  $V_2$  and  $I_o$  in the following circuit [Show analysis using Cramer's rule to calculate the voltage at node 2]. [CO3, C4, Mark: 4]



4. Using source transformation, **find**  $V_x$  in the following circuit.

[CO3, C4,  
EP1,  
Mark:4]

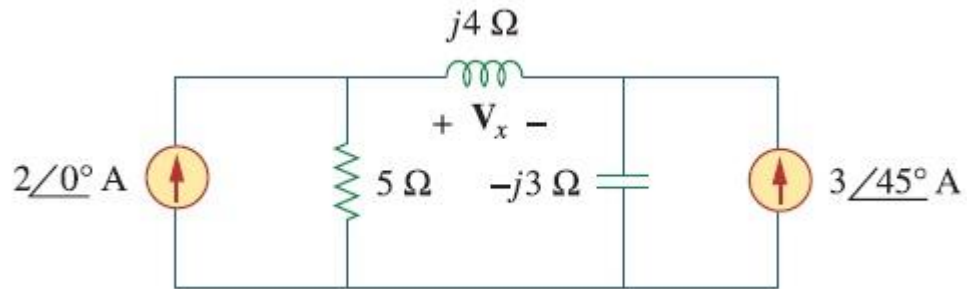

5. **Find** the value of  $Z_L$  that will absorb the maximum power and the value of the maximum power in the following circuit.

[CO3, C4,  
EP1, EP2,  
Mark:6]

