



EAST WEST UNIVERSITY
Department of Computer Science and Engineering
B.Sc. in Computer Science and Engineering Program
Final Exam, Summer 2021 Semester

Course: CSE 109/209 Electrical Circuits, Section-4
Instructor: M Saddam Hossain Khan, Senior Lecturer, CSE Department
Full Marks: 20 (20 will be counted for final grading)
Time: 1 Hour and 30 Minutes (Including submission)

Note: There are FIVE problems, answer ALL of them. Course Outcome (CO), Cognitive Level and Mark of each question are mentioned at the right margin.

1. Determine $V(t)$ and $I(t)$ in the following circuit.

[CO1,C2,
Mark:3]


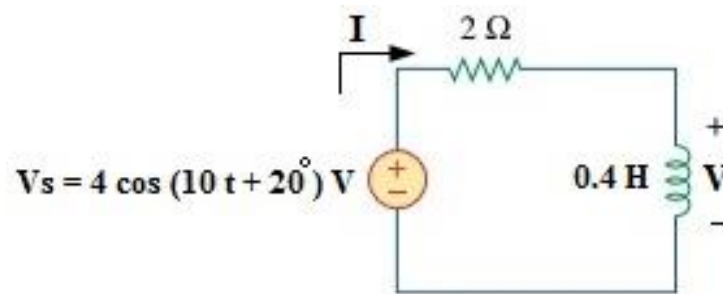


Figure 1


2. Determine Z_{eq} and I for the following circuit.

[CO1,C2,
Mark: 3]

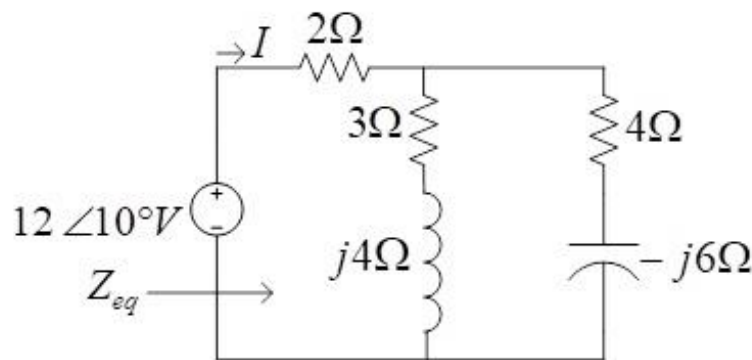


3. Using nodal analysis, compute V_1 for the following circuit [Show analysis using Cramer's rule].

[CO3,C4,
Mark: 4]

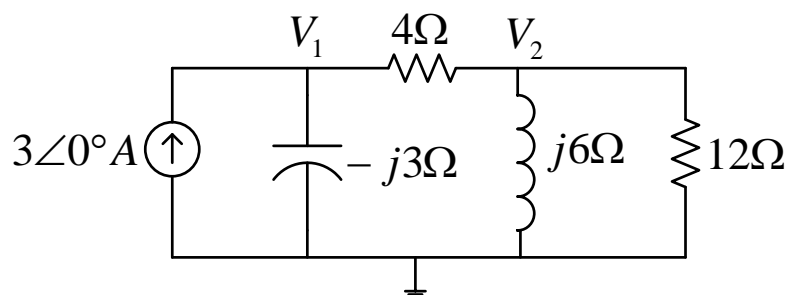


4. Using the superposition principle, **find** i_x in the following circuit.

[CO3,C4,
Mark:4]

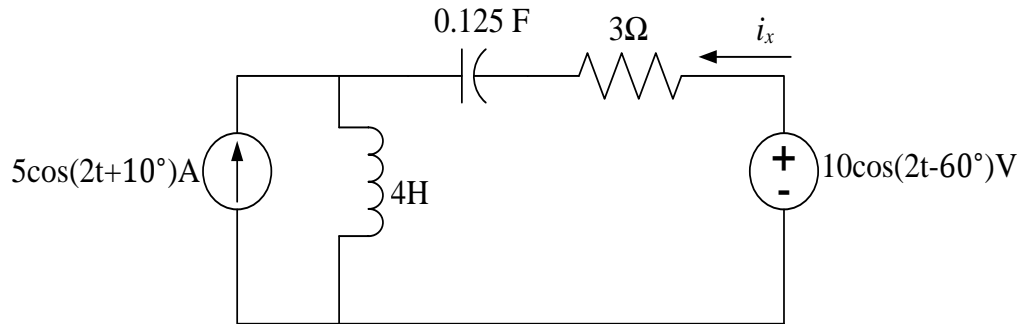

5. a) **Find** the value of Z_L that will absorb the maximum power and the value of the maximum power in the following circuit.

[CO3,C4,
Mark:6]

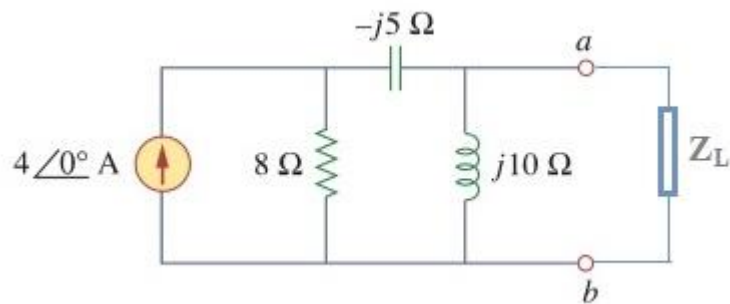

- b) **Find** the average power supplied by the source and absorbed by the resistor from Figure 1.