



## **Lab Report: Electrical Circuits (CSE 209)**

**Expt. No: 07**

**Title: Verification of Thevenin's theorem.**

**Submitted by-**

Name: Md.Minhajur Rahman

ID: 2023-3-60-301

Section- 01

Group- 05

**Submitted to-**

Dr. Sarwar Jahan

Associate Professor

Department of Computer Science & Engineering

East West University

**Date of Performance:** 24/12/24

**Date of Submission:** 02/01/25

**Objectives:**

1. Verifying the Thevenin's theorem theoretically, experimentally, and using PSpice simulation.

**Theory:**

Circuit containing a voltage source  $E_{th}$  in series with a resistance  $R_{th}$ .  $E_{th}$  is equal to the open circuit voltage between the terminals and  $R_{th}$  is the ratio of the open circuit voltage to the short circuit current through the terminals. Experimentally,  $E_{th}$  may be measured by measuring Thevenin's theorem states that a linear two-terminal network can be replaced by an equivalent open circuit voltage and  $R_{th}$  can be calculated by measuring the open circuit voltage and the short circuit current.

Circuit Diagram:

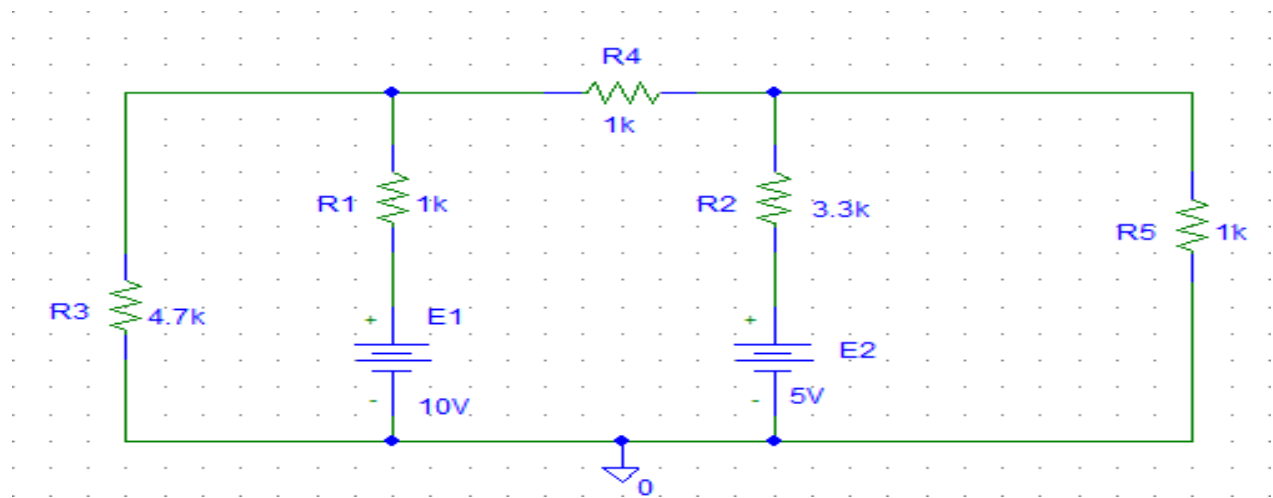


Figure 1: Circuit Diagram whose Thevenin's equivalent to be determined

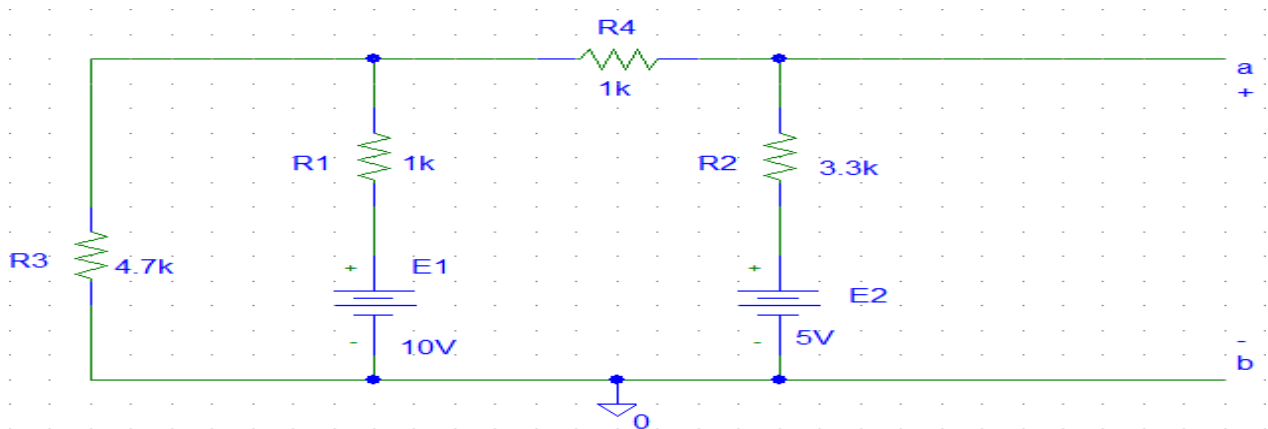


Figure 2: Circuit Diagram to measure the open circuit voltage.

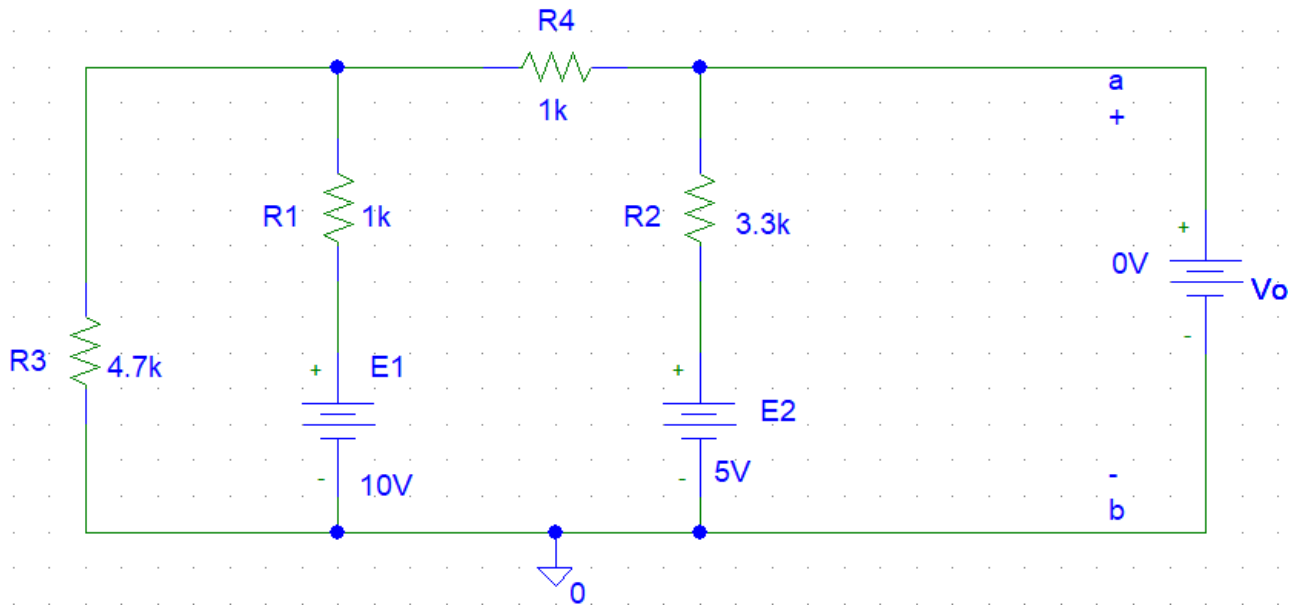


Figure 3: Circuit Diagram to measure the short circuit current.


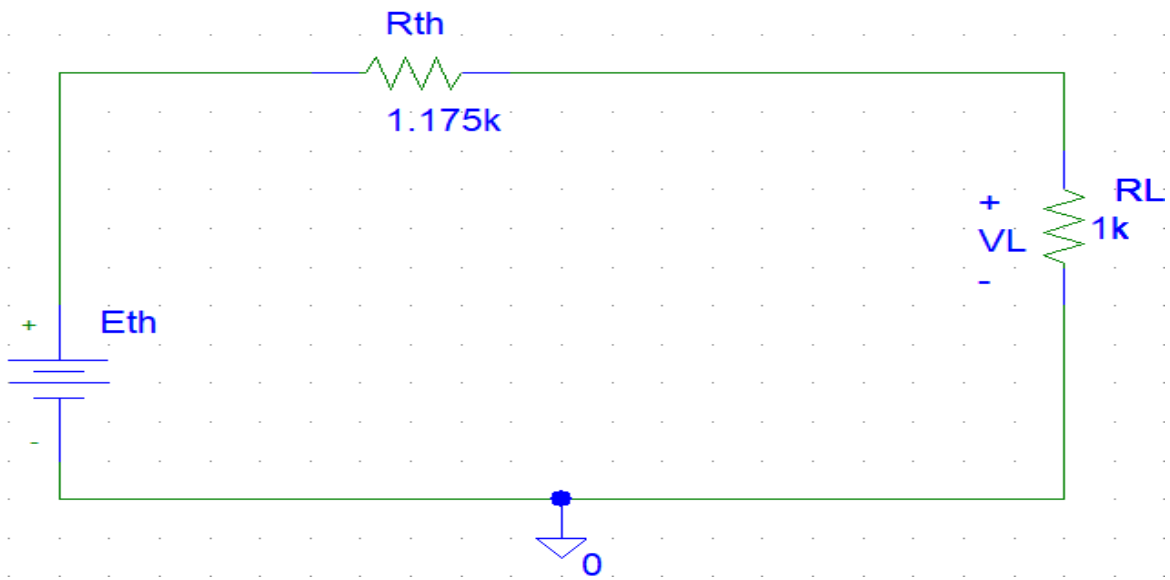


Figure 4: Circuit Diagram to verify Thevenin's theorem.

**Pre-lab report question:**

1. Theoretically calculate  $V_L$  and  $I_L$  in figure 1. Then theoretically calculate  $V_{oc}$  in figure 2 and  $I_{sc}$  in figure 3. From the values of  $V_{oc}$  and  $I_{sc}$ , determine  $E_{th}$  and  $R_{th}$ . Theoretically calculate  $V_L$  and  $I_L$  in figure 4. Verify the Thevenin's theorem from calculated data.

**Answer:**

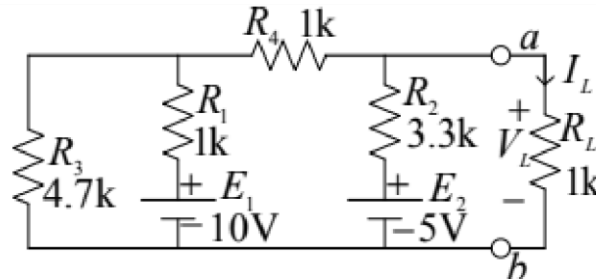

**Circuit from the manual Figure: 01**

Applying KVL at mesh 1, 2 and 3,

$$(5.7k)i_1 - (1k)i_2 = -10 \dots (1)$$


$$-(1k)i_1 + (5.3k)i_2 - (3.3k)i_3 = 10 - 5 \dots (2)$$

$$-(3.3k)i_2 + (4.3k)i_3 = 5 \dots (3)$$

By solving equation (1), (2) and (3) we get,

$$i_3 = I_L = 3.26 \text{ mA}$$

Again,

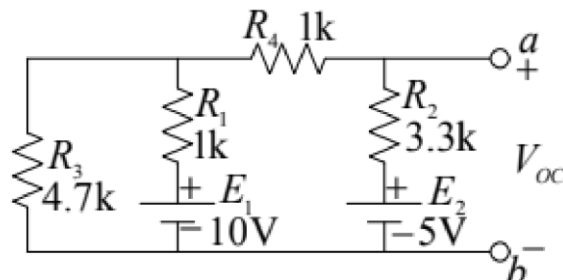

**Circuit from the manual Figure: 02**

Applying KVL a mesh 1 and 2 we get,

$$(5.7k)i_1 - (1k)i_2 = -10 \dots (1)$$

$$(1k)i_1 + (5.3k)i_2 = 10 - 5 \dots (2)$$

By solving,


$$i_2 = 0.633 \text{ mA}$$

Here,

$$V_{oc} = E_{th} = (3.3k)i_2 + 5$$

$$\text{So, } E_{th} = 7.09 \text{ V}$$

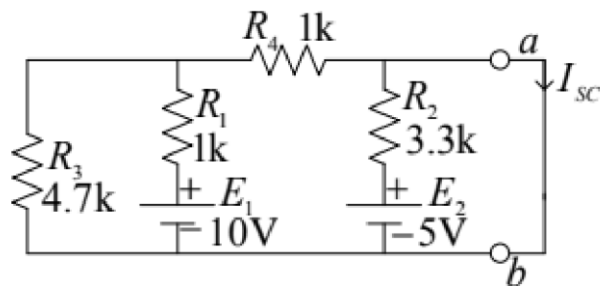After disconnecting the load and replaced with short circuit,



**Circuit from the manual Figure: 03**

Here,

$$i_3 = I_{sc}$$

Applying KVL at mesh 1, 2 and 3,

$$(5.7k)i_1 - (1k)i_2 = -10 \dots (1)$$

$$(1k)i_1 + (5.3k)i_2 - (3.3k)i_3 = 10 - 5 \dots (2)$$

$$(3.3k)i_2 + (3.3k)i_3 = 5 \dots (3) \quad \text{By}$$


solving equation (1), (2) and (3) we get,

$$i_3 = I_{sc} = 6.034 \text{ mA}$$

So,

$$R_{th} = \frac{V_{th}}{I_{sc}} = \frac{7.09}{0.006034} = 1175 \, \Omega$$

The Thevenin's equivalent circuit,

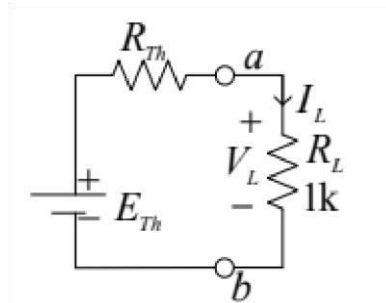

**Circuit from the manual Figure: 04**

So,

$$I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{7.09}{1.175} = 3.26 \text{mA}$$

### Experimental Data sheet:

**Table 1.** Experimental Datasheet for determining Thevenin's equivalent circuit.

Measured Value of $E_1$	Measured Value of $E_2$	Measured Value of $V_L$	Measured Value of $I_L$	Measured value of $V_{OC}$	Measured value of $I_{SC}$	Measured values of resistors ( $k\Omega$ )
9.927 ✓	5.005 ✓	3.241	3.2mA	7.075V	6.00mA	$R_1 = 0.980$ $R_2 = 3.333$ $R_3 = 4.633$ $R_4 = 0.993$ $R_L = 0.982$


**Table 2.** Experimental Datasheet for Thevenin's equivalent circuit.

$E_{th} = V_{OC}$	$R_{th} = V_{OC}/I_{SC}$	Measured Value of $V_L$	Measured Value of $I_L$
7.075	1.162	3.3	3.27 mA

### Answer of the post lab question:

1. Theoretically calculate  $V_L$  and  $I_L$  in Figure 1 using measured values of  $E_1$ ,  $E_2$ ,  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_4$ , and  $R_L$ . Then theoretically calculate VOC in Figure 2 and ISC in Figure 3 using measured values of  $E_1$ ,  $E_2$ ,  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_4$ , and  $R_L$ . From the values of VOC and ISC, determine  $E_{Th}$  and  $R_{Th}$ . Theoretically calculate  $V_L$  and  $I_L$  in Figure 4 using calculated values of  $E_{Th}$  and  $R_{Th}$  and the measured value of  $R_L$ . Verify the Thevenin's theorem from calculated data.

### Answer:

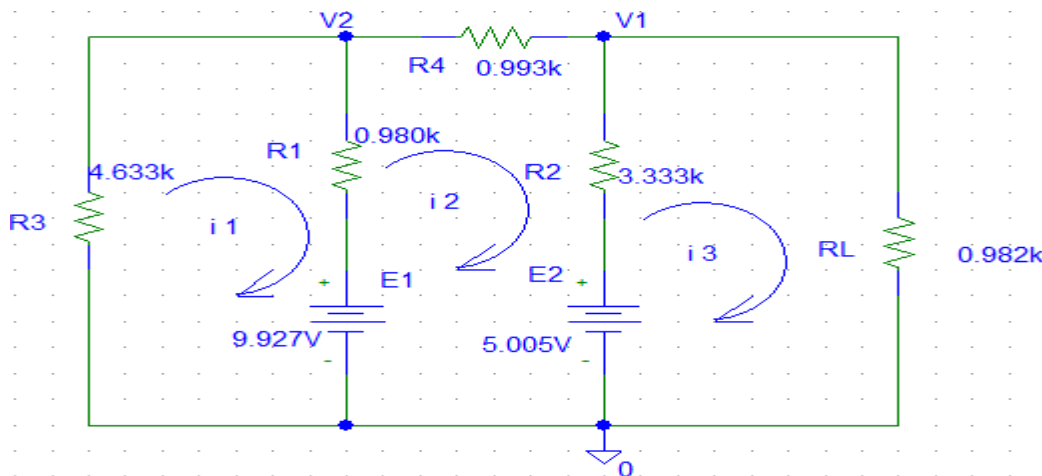

#### KVL at mesh 1:

$$4.633i_1 + 0.980(i_1 - i_2) = -9.927$$

$$5.613i_1 - 0.980i_2 = -9.927 \dots \dots \dots (1)$$

#### KVL at mesh 2

$$0.980(i_2 - i_1) + 0.993i_2 + 3.333(i_2 - i_3) = 9.927 - 5.005$$

$$\Rightarrow -0.980i_1 + 5.306i_2 - 3.333i_3 = 4.922 \dots \dots \dots (2)$$

#### KVL at mesh 3:

$$3.333(i_3 - i_2) + 0.982i_3 = 5.005$$

$$\Rightarrow -3.333i_2 + 4.315i_3 = 5.005 \dots \dots \dots (3)$$


$$i_1 = -1.288 \text{ mA}$$

$$i_2 = 2.755 \text{ mA}$$

$$i_3 = 3.288 \text{ mA}$$

$$I_L = 3.288 \text{ mA}$$
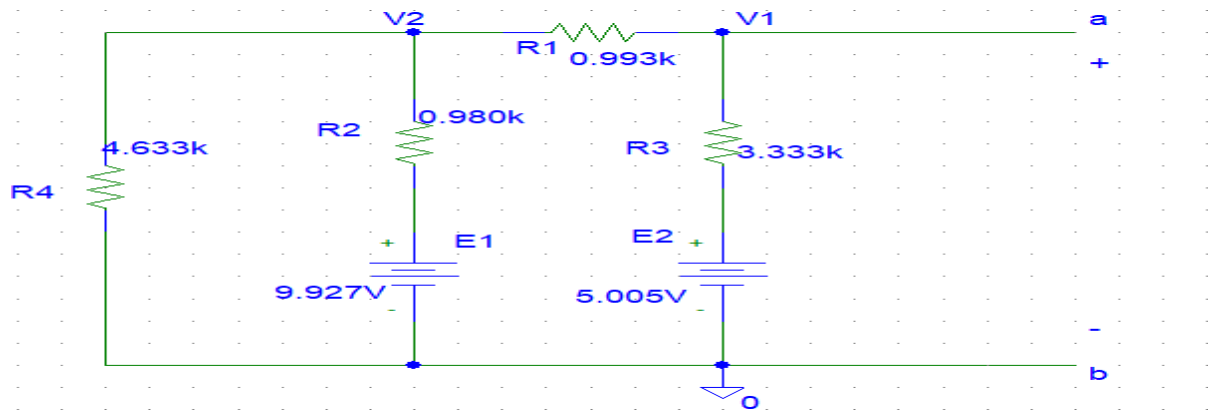
$$\begin{aligned} V_L &= 3.288 \times 0.982 \text{ V} \\ &= 3.230 \text{ V} \end{aligned}$$



**KCL at node 2:**

$$\frac{V_2}{4.633} + \frac{V_2 - 9.927}{0.980} + \frac{V_2 - V_1}{0.993} = 0$$


$$-1.007v_1 + 2.2433v_2 = 10.129 \dots \dots (1)$$

**KCL at node 1:**

$$\frac{V_1 - V_2}{0.993} + \frac{V_1 - 5.005}{3.333} = 0$$

$$1.307v_1 - 1.007v_2 = 1.5016 \dots \dots (2)$$
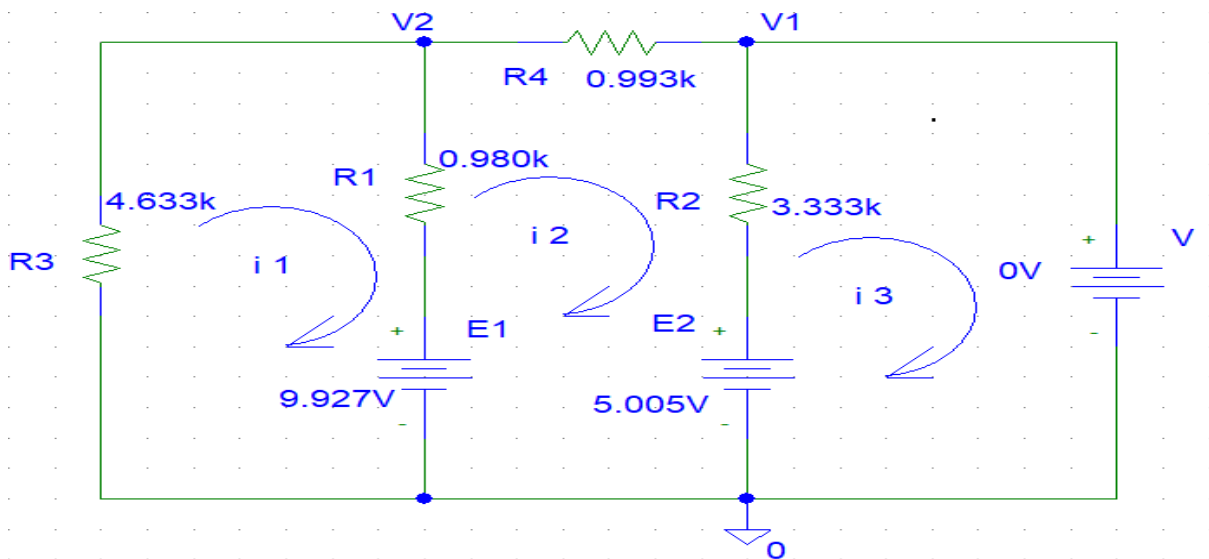
$$\text{So, } v_1 = v_{oc} = v_{th} = 7.075v$$





**KVL at mesh 1:**

$$4.633i_1 + 0.980(i_1 - i_1) = -9.927$$

$$5.613i_1 - 0.980i_2 = -9.927 \dots \dots (1)$$

**KVL at mesh 2:**

$$0.980(i_2 - i_1) + 0.993i_2 + 3.333(i_2 - i_3) = 9.927 - 5.005$$

$$\Rightarrow -0.980i_1 + 5.306i_2 - 3.333i_3 = 4.922 \dots \dots (2)$$

**KVL at mesh 3:**

$$3.333(i_3 - i_2) = 5.005$$


$$\Rightarrow -3.333i_2 + 3.333i_3 = 5.005 \dots \dots (3)$$

$$i_1 = -0.975mA$$

$$i_2 = 4.547mA$$

$$i_3 = 6.049mA$$

$$i_3 = i_{sc} = 6.049mA$$

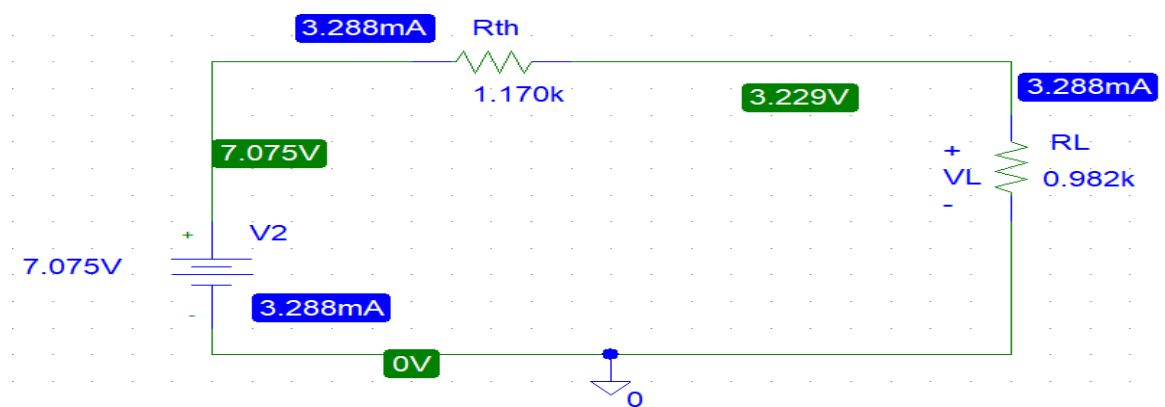

$$E_{th} = v_{oc} = 7.075v$$

$$R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{7.075}{6.049} = 1.170k \text{ ohm}$$

$$V_L = \frac{7.075}{1.170+0.982} * 0.982$$

$$V_L = 3.230 v$$

$$I_L = \frac{3.230}{0.982}$$

$$= 3.288mA$$

Here we see that,  $V_L$  and  $I_L$  from figure 1 is equal to the  $V_L$  and  $I_L$  of figure 4. So Thevenin's theorem is verified.

2. Compare the measured values and the calculated values from step 1 and comment on any observed discrepancy:


Measure d value of $V_L$	Calculat ed value of $V_L$	Measure d value of $I_L(\text{mA})$	Calculat ed ed value of $I_L (\text{mA})$	Measure d value of $V_{oc}$	Calculat ed value of $V_{oc}$	Measured value of $I_{sc}(\text{mA})$	Calculated value of $I_{sc}$ (mA)
3.241V	3.230 V	3.2mA	3.288	7.075 V	7.075V	6.00	6.049

In the Above table we see that, the measured value of  $V_L$  is 3.241V and the calculated value of  $V_L$  is 3.230V. Both values are close. The measured value of  $I_L$  is 3.2mA and the calculated value of  $I_L$  is 3.288mA. Both values are also the same. The measured value of  $V_{oc}$  is the same as the calculated value of  $V_{oc}$ . The measured value of  $I_{sc}$  and the calculated value if  $I_{sc}$  are also very close to each other.

3. Using PSpice, simulate the circuit of Figure 1 and determine  $V_L$  and  $I_L$ . Simulate the circuit of Figure 2 and determine  $V_{OC}$ . For this purpose, connect a 0A current source between nodes a and b. Simulate the circuit of Figure 3 and determine  $I_{SC}$ . For this purpose, connect a 0V voltage source between nodes a and b. Determine the values of  $E_{th}$  and  $R_{th}$ . Simulate the circuit of Figure 4 and determine  $V_L$  and  $I_L$ . Verify the Thevenin's theorem from simulated data.


Answer:

PSpice simulation circuit of figure 1:

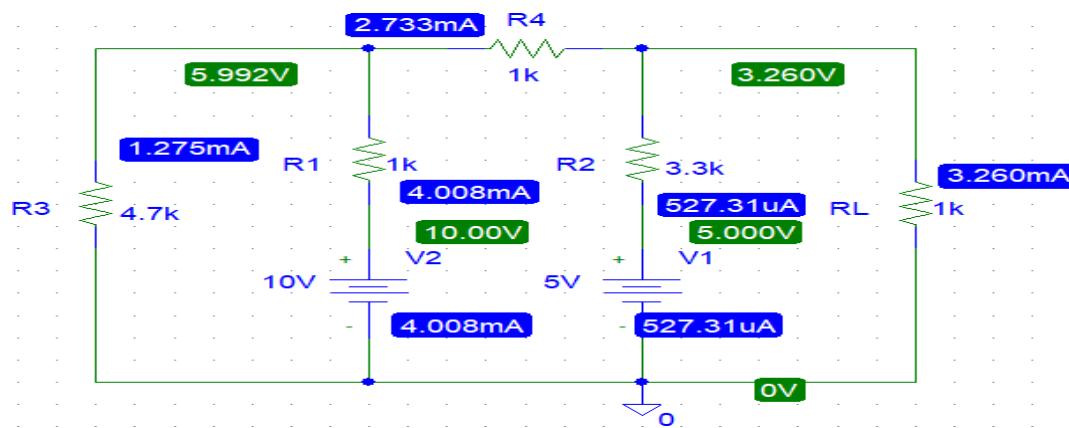


Here the value of  $V_L = 3.260V$  And the value of  $I_L = 3.260mA$

PSpice simulation circuit of figure 2:

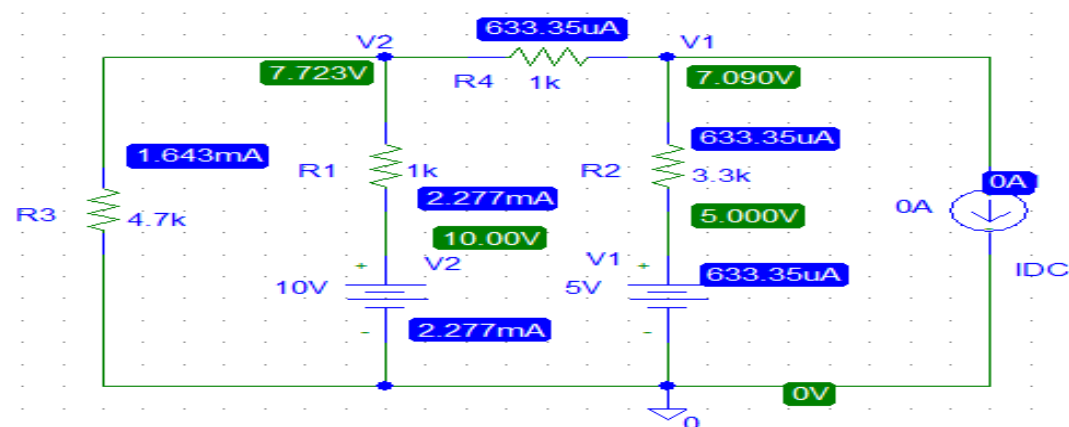

Here the value of  $V_{oc} = v1 = 7.090v$

PSpice simulation circuit of figure 3:

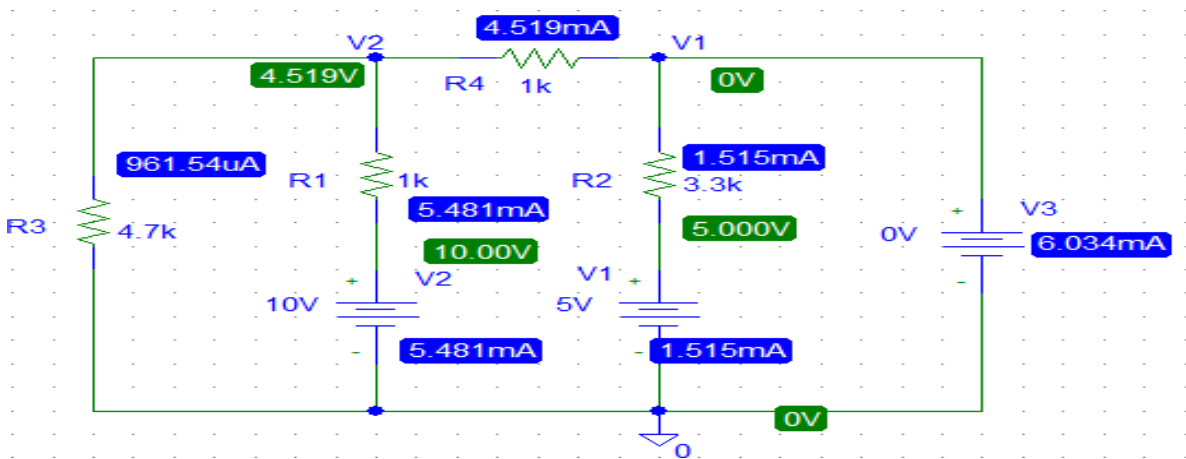


Here the value of  $I_{sc}=6.034\text{mA}$

$$E_{th} = v_{oc} = 7.090\text{V}$$

$$R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{7.090}{6.034} = 1.175\text{k ohm}$$

PSpice simulation circuit of figure 4:

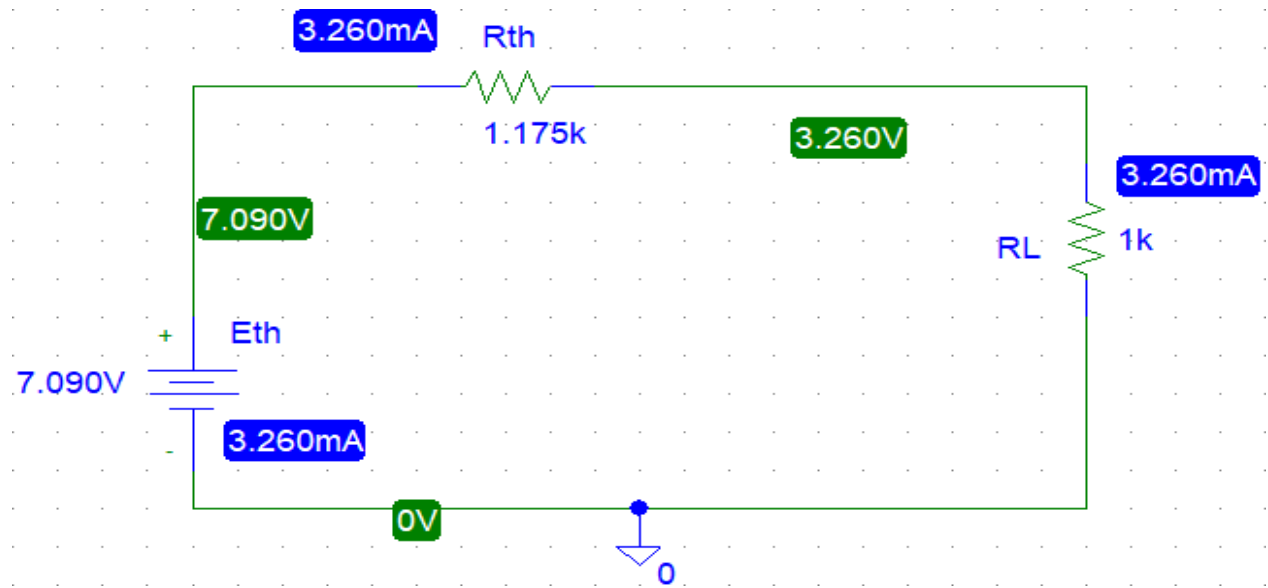

Here we see that,  $V_L$  and  $I_L$  from figure 1 is equivalent to the  $V_L$  and  $I_L$  of figure 4. So Thevenin's theorem is verified.

### Discussions:

1. It is needed to be ensured that all the connections are established according to the given circuit in the manual.
2. When measuring Thevenin resistance, it is needed to make sure that voltage sources are shorted and current sources are open to avoid incorrect resistance readings.
3. Same load resistance should be used for both the original circuit and the Thevenin equivalent circuit to ensure fair comparison of result.
4. It should be ensured that the circuit is correctly grounded to prevent any interference from affecting the result.